


Experiment 7

Aim: Write Verilog codes to create T flip flop, SR flip flop, D flip flop and verify it using a testbench.

Theory:

T Flip-Flop (Toggle Flip-Flop):

 The T flip-flop is also known as a toggle flip-flop because it toggles its output (Q) based on the input (T). Here's the truth table for a T flip-flop:




	Previous		Next	
T	Q	Q'	Q	Q'
0	0	1	0	1
0	1	0	1	0
1	0	1	1	0
1	1	0	0	1

SR Flip-Flop (Set-Reset Flip-Flop):


The SR flip-flop has two inputs, S (Set) and R (Reset). It can be used to set (S=1) or reset (R=1) the flip-flop. Here's the truth table:

SR Flip Flop By NAND Gate

 

Truth Table of SR Flip Flop


S	R	Q	Q'
0	0	0	1
0	1	0	1
1	0	1	0
1	1	∞	∞

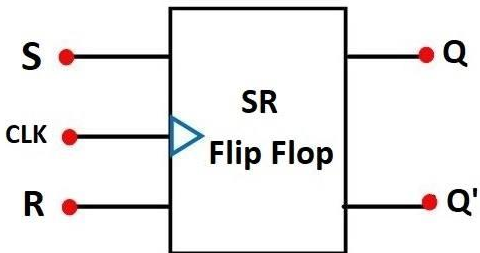

The diagram shows a block labeled 'SR Flip Flop'. It has three inputs on the left: 'S', 'CLK', and 'R'. The 'CLK' input is marked with a blue triangle symbol, indicating a clock input. It has two outputs on the right: 'Q' and 'Q''. Red dots are placed at each input and output connection point.

D Flip-Flop (Data Flip-Flop):

 The D flip-flop has a single data input (D) and a clock input (CLK). It stores the value of the D input on the rising edge of the clock signal. Here's the truth table:



Clock	D	Q	Q'	Description
↓ » 0	X	Q	Q'	Memory no change
↑ » 1	0	0	1	Reset Q » 0
↑ » 1	1	1	0	Set Q » 1

Code:**Behavioural Verilog code for T flip flop:**

```
module TFF(
    input CLK,
    input T,
    input reset,
    output Q,
    output Q_bar
);

    reg Q, Q_next;

    always @(posedge CLK or posedge reset) begin
        if (reset) begin
            Q <= 1'b0;
        end else begin
            Q <= T ? ~Q : Q;
        end
    end

    assign Q_bar = ~Q;

endmodule
```

Testbench for T flip flop:

```
module testbench_TFF;

    reg CLK;
    reg T;
    reg reset;
    wire Q;
    wire Q_bar;

    // Instantiate the T flip-flop
    TFF UUT (
        .CLK(CLK),
        .T(T),
        .reset(reset),
        .Q(Q),
        .Q_bar(Q_bar)
    );

    initial begin
        // Initialize inputs
    end

endmodule
```

```

CLK = 0;
T = 0;
reset = 0;

// Apply a reset pulse
reset = 1;
#10 reset = 0;

// Test cases
#5 T = 1; // Toggling input, Q should change
#5 T = 0; // T is 0, Q should remain the same
#5 T = 1; // Toggling input again, Q should change


// Test cases
#5 T = 1; // Toggling input, Q should change
#5 T = 0;
#5 T = 1;
$finish;
end

always begin
    #5 CLK = ~CLK; // Toggle the clock every 5 time units
end


endmodule

```


RTL Schematic:

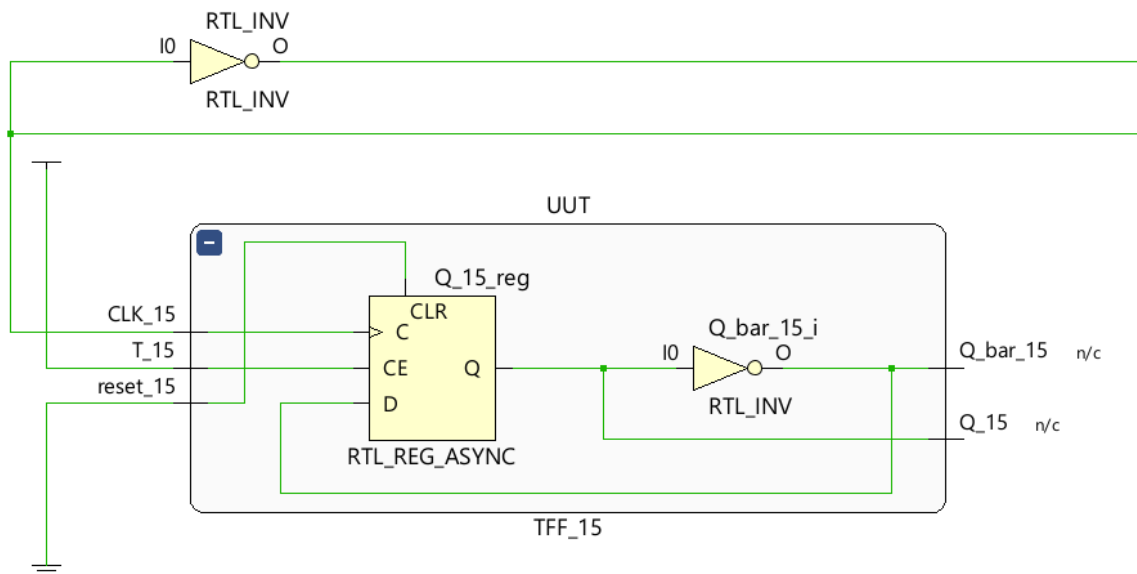

Function Verification:

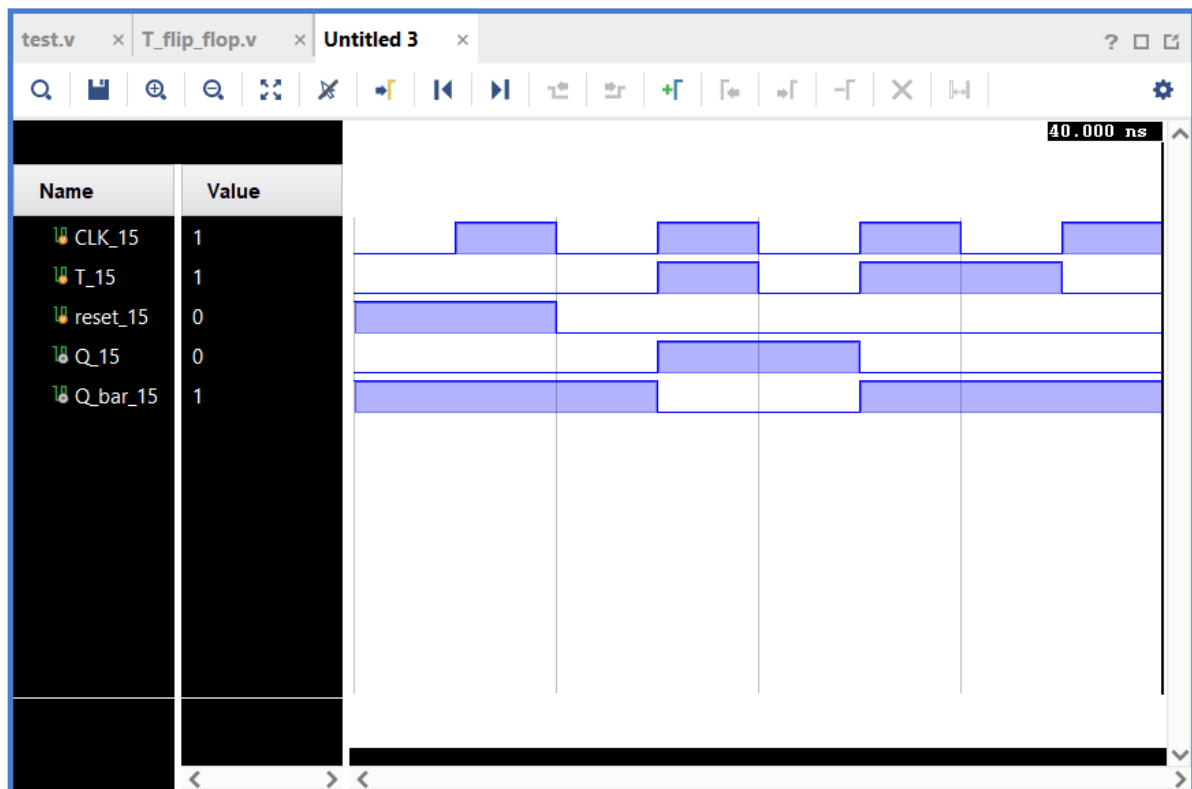

Post synthesis schematic:

 


Post power report:

Summary

Power estimation from Synthesized netlist. Activity derived from constraints files, simulation files or vectorless analysis. Note: these early estimates can change after implementation.

Total On-Chip Power: 2.106 W
Design Power Budget: Not Specified
Process: typical
Power Budget Margin: N/A
Junction Temperature: 29.0°C
 Thermal Margin: 56.0°C (29.6 W)
 Ambient Temperature: 25.0 °C
 Effective θ_{JA} : 1.9°C/W
 Power supplied to off-chip devices: 0 W

On-Chip Power

 


Post synthesis timing summary:

Unconstrained Paths - NONE - NONE - Setup


Name	Slack	Levels	Routes	High Fanout	From	To	Total Delay	Logic Delay	Net Delay	Requirement	Source Clock
Path 1	∞	3	3	3	Q_15_reg/C	Q_bar_15	3.730	2.887	0.844	∞	
Path 2	∞	2	2	3	Q_15_reg/C	Q_15	3.419	2.836	0.584	∞	
Path 3	∞	2	3	1	T_15	Q_15_reg/D	1.466	0.883	0.584	∞	input port clock
Path 4	∞	1	2	1	reset_15	Q_15_reg/CLR	1.413	0.830	0.584	∞	input port clock

Post utilization/ area summary:

Resource	Utilization	Available	Utilization %
LUT	1	41000	0.00
FF	1	82000	0.00
IO	5	300	1.67

 

Post implementation schematic:

 


Post implementation power report:

Summary

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power:	2.042 W
Design Power Budget:	Not Specified
Process:	typical
Power Budget Margin:	N/A
Junction Temperature:	28.8°C
Thermal Margin:	56.2°C (29.6 W)
Ambient Temperature:	25.0 °C
Effective θ_{JA} :	1.9°C/W
Power supplied to off-chip devices:	0 W


On-Chip Power

 

Post implementation timing summary:

Unconstrained Paths - NONE - NONE - Setup

Name	Slack	Levels	Routes	High Fanout	From	To	Total Delay	Logic Delay	Net Delay	Requirement	Source Clock
Path 1	∞	3	2	3	Q_15_reg/C	Q_bar_15	4.367	2.773	1.595	∞	
Path 2	∞	2	1	3	Q_15_reg/C	Q_15	4.008	2.703	1.305	∞	
Path 3	∞	1	1	1	reset_15	Q_15_reg/CLR	1.644	0.787	0.856	∞	input port clock
Path 4	∞	2	1	1	T_15	Q_15_reg/D	1.559	0.870	0.689	∞	input port clock

 Post implementation utilization/ area summary:**Code:****Behavioural Verilog code for SR flip flop:**

```

module sr_flip_flop (
    input CLK,
    input S,
    input R,
    output Q,
    output Q_bar
);

reg Q, Q_bar;

always @(posedge CLK) begin
    if (R && S) begin
        // Invalid condition, both set and reset are active
        Q <= 1'b0;
        Q_bar <= 1'b1;
    end else if (R) begin
        // Reset is active
        Q <= 1'b0;
        Q_bar <= 1'b1;
    end else if (S) begin
        // Set is active
        Q <= 1'b1;
        Q_bar <= 1'b0;
    end else begin
        // No action
    end
end

```

```
        Q <= Q;
        Q_bar <= Q_bar;
    end
end

endmodule
```

Testbench for SR flip flop:

```
module testbench;




    reg CLK;
    reg S;
    reg R;
    wire Q;
    wire Q_bar;

    sr_flip_flop uut (
        .CLK(CLK),
        .S(S),
        .R(R),
        .Q(Q),
        .Q_bar(Q_bar)
    );

    initial begin
        CLK = 0;
        S = 0;
        R = 0;
        #5 R = 1;
        #5 S = 1;
        #5 R = 0;
        #5 S = 0;
        #5 R = 1;
        #5 S = 1;
        #5 R = 0;
        #5 S = 0;
        #5 $finish;
    end

    always begin
        #2 CLK = ~CLK;
    end

endmodule
```

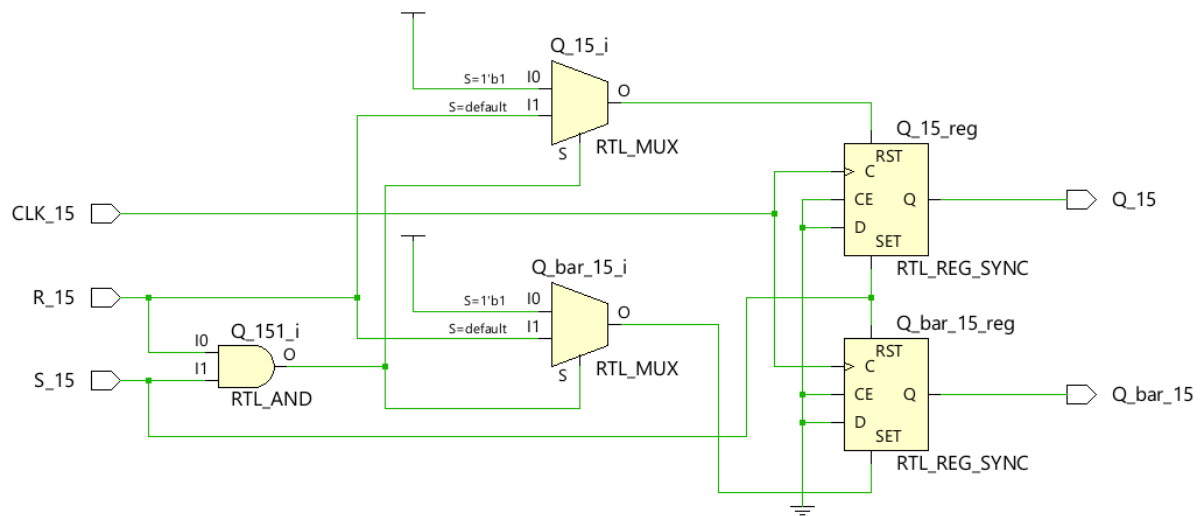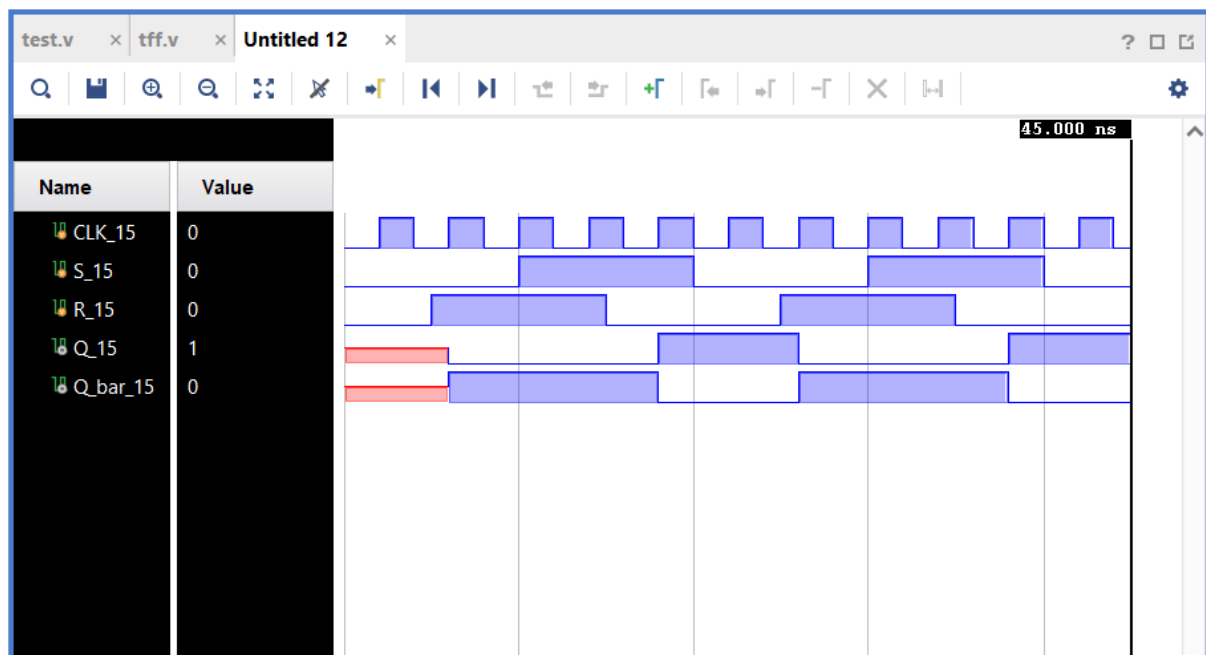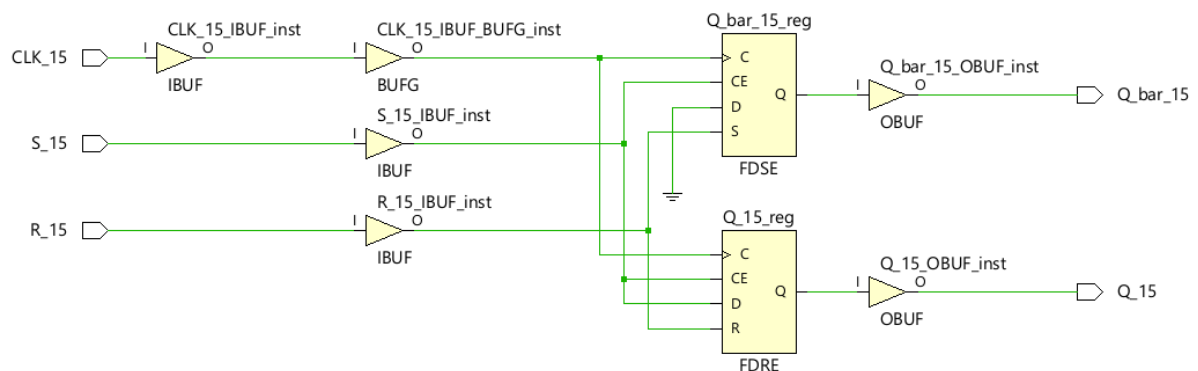
RTL Schematic:**Function Verification:****Post synthesis schematic:**


Post power report:

Summary

Power estimation from Synthesized netlist. Activity derived from constraints files, simulation files or vectorless analysis. Note: these early estimates can change after implementation.

Total On-Chip Power: 0.116 W
Design Power Budget: Not Specified
Process: typical
Power Budget Margin: N/A
Junction Temperature: 25.2°C
 Thermal Margin: 59.8°C (31.5 W)
 Ambient Temperature: 25.0 °C
 Effective θ_{JA} : 1.9°C/W

On-Chip Power

 


Post synthesis timing summary:


Name	Slack	Levels	Routes	High Fanout	From	To	Total Delay	Logic Delay	Net Delay	Requirement	Source Clock
Path 1	∞	2	2	1	Q_15_reg/C	Q_15	3.419	2.836	0.584	∞	
Path 2	∞	2	2	1	Q_bar_15_reg/C	Q_bar_15	3.419	2.836	0.584	∞	
Path 3	∞	1	2	3	S_15	Q_15_reg/CE	1.413	0.830	0.584	∞	input port clock
Path 4	∞	1	2	3	S_15	Q_15_reg/D	1.413	0.830	0.584	∞	input port clock
Path 5	∞	1	2	2	R_15	Q_15_reg/R	1.413	0.830	0.584	∞	input port clock
Path 6	∞	1	2	3	S_15	Q_bar_15_reg/CE	1.413	0.830	0.584	∞	input port clock
Path 7	∞	1	2	2	R_15	Q_bar_15_reg/S	1.413	0.830	0.584	∞	input port clock

Post utilization/ area summary

Resource	Utilization	Available	Utilization %
FF	2	82000	0.00
IO	5	300	1.67

 

Post implementation schematic:

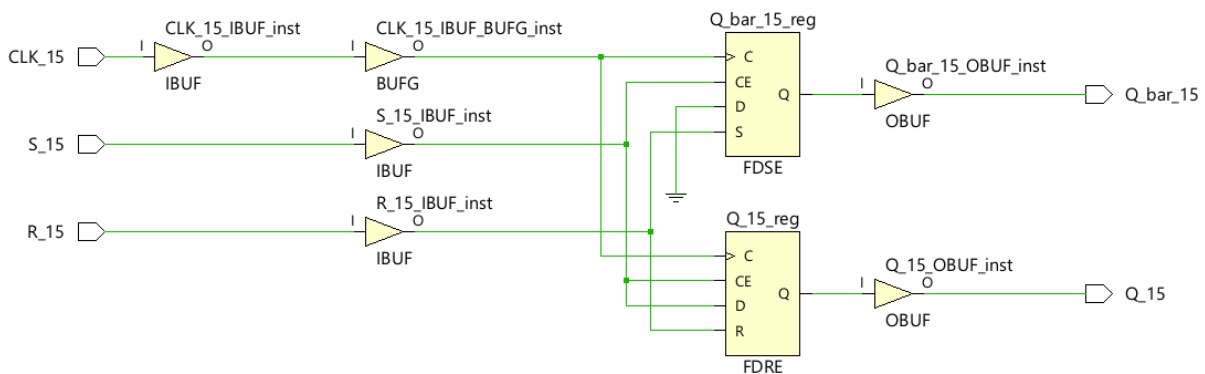


Post implementation power report:

Summary

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power: 0.119 W
Design Power Budget: Not Specified
Process: typical
Power Budget Margin: N/A
Junction Temperature: 25.2°C
 Thermal Margin: 59.8°C (31.5 W)
 Ambient Temperature: 25.0 °C
 Effective θ_{JA} : 1.9°C/W
 Power supplied to off-chip devices: 0 W

On-Chip Power

 


Post implementation timing summary:

Name	Slack	Levels	Routes	High Fanout	From	To	Total Delay	Logic Delay	Net Delay	Requirement	Source Clock
↳ Path 1	∞	2	1	1	Q_15_reg/C	Q_15	3.997	2.703	1.295	∞	
↳ Path 2	∞	2	1	1	Q_bar_15_reg/C	Q_bar_15	3.991	2.720	1.272	∞	
↳ Path 3	∞	1	1	3	S_15	Q_15_reg/D	1.669	0.787	0.881	∞	input port clock
↳ Path 4	∞	1	1	2	R_15	Q_15_reg/R	1.570	0.814	0.756	∞	input port clock
↳ Path 5	∞	1	1	2	R_15	Q_bar_15_reg/S	1.570	0.814	0.756	∞	input port clock
↳ Path 6	∞	1	1	3	S_15	Q_15_reg/CE	1.522	0.787	0.734	∞	input port clock
↳ Path 7	∞	1	1	3	S_15	Q_bar_15_reg/CE	1.522	0.787	0.734	∞	input port clock

Post implementation utilization/ area summary:

Resource	Utilization	Available	Utilization %
FF	2	82000	0.00
IO	5	300	1.67

 

Code:

Behavioural Verilog code for D flip flop:

```
module d_flip_flop (
    input CLK,
    input D,
    input en,
    output Q,
    output Q_bar
);

reg Q, Q_bar;

always @(posedge CLK) begin
```

```
        if (en) begin
            Q <= D;
            Q_bar <= ~D;
        end
    end

endmodule
```

Testbench for D flip flop:

```
module testbench;




    reg CLK;
    reg D;
    reg en;
    wire Q;
    wire Q_bar;

    d_flip_flop uut (
        .CLK(CLK),
        .D(D),
        .en(en),
        .Q(Q),
        .Q_bar(Q_bar)
    );

    initial begin
        CLK = 0;
        D = 0;
        en = 0;
        #5 en = 1;
        #5 D = 1;
        #5 D = 0;
        #5 D = 1;
        #5 en = 0;
        #5 $finish;
    end

    always begin
        #2 CLK = ~CLK;
    end

endmodule
```

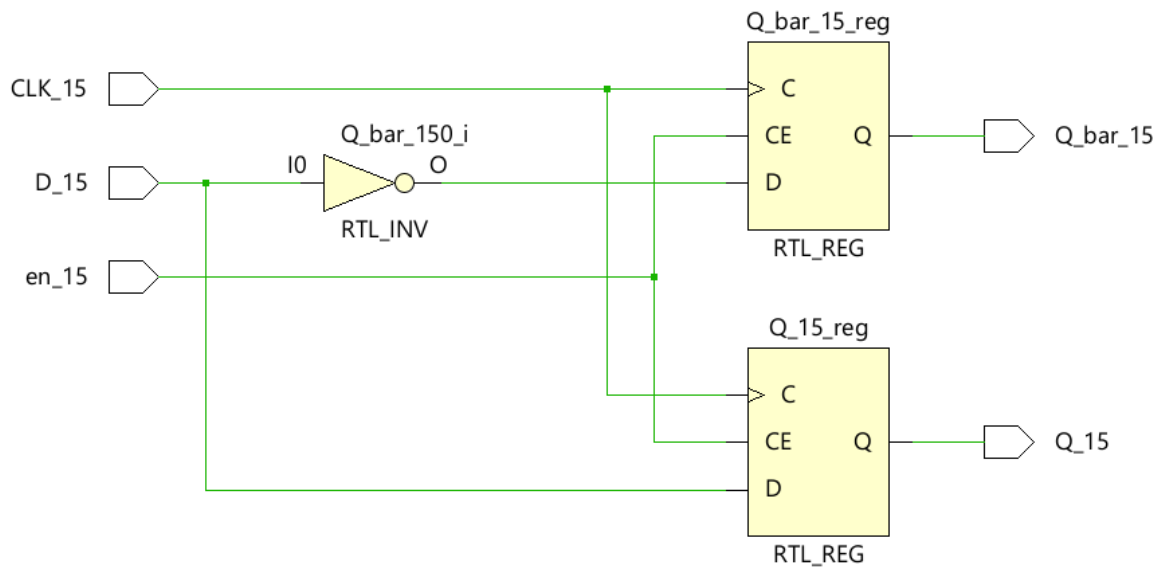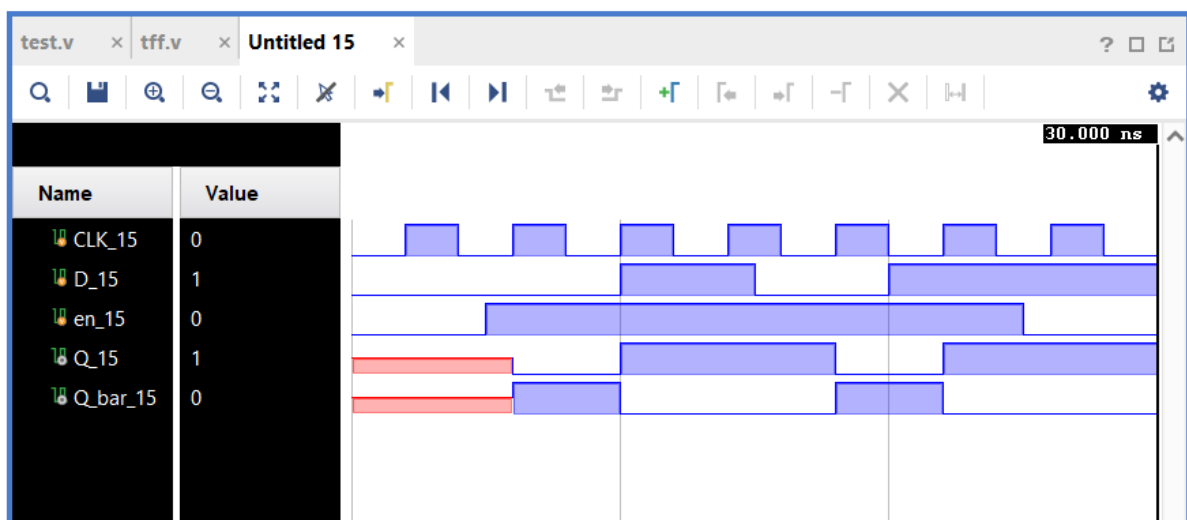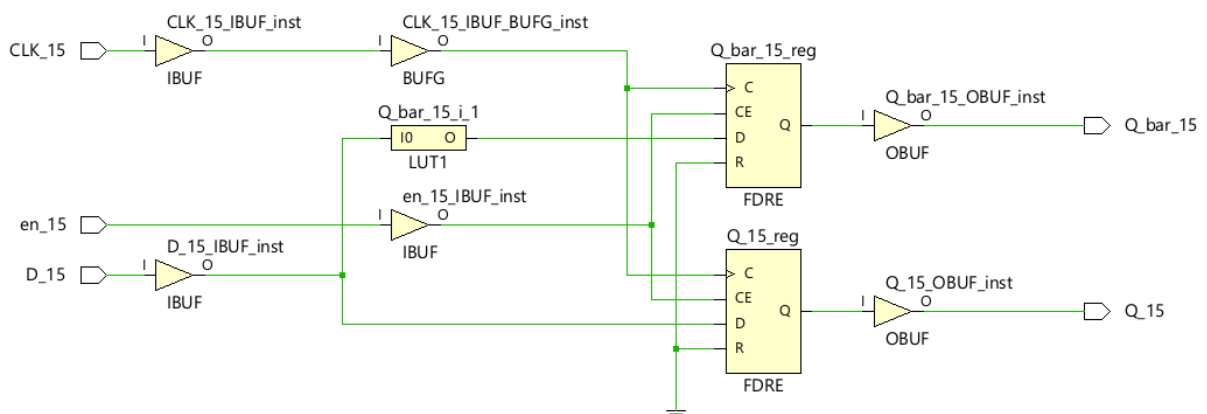RTL Schematic:**Function Verification:****Post synthesis schematic:**


Post power report:

Summary

Power estimation from Synthesized netlist. Activity derived from constraints files, simulation files or vectorless analysis. Note: these early estimates can change after implementation.

Total On-Chip Power: **0.595 W**
Design Power Budget: **Not Specified**
Process: **typical**
Power Budget Margin: **N/A**
Junction Temperature: **26.1 °C**
 Thermal Margin: 58.9 °C (31.1 W)
 Ambient Temperature: 25.0 °C
 Effective θ_{JA} : 1.9 °C/W
 Power supplied to off-chip devices: 0 W

On-Chip Power

 


Post synthesis timing summary:


Name	Slack	Levels	Routes	High Fanout	From	To	Total Delay	Logic Delay	Net Delay	Requirement	Source Clock
Path 1	∞	2	2	1	Q_15_reg/C	Q_15	3.419	2.836	0.584	∞	
Path 2	∞	2	2	1	Q_bar_15_reg/C	Q_bar_15	3.419	2.836	0.584	∞	
Path 3	∞	2	3	2	D_15	Q_bar_15_reg/D	1.466	0.883	0.584	∞	input port clock
Path 4	∞	1	2	2	en_15	Q_15_reg/CE	1.413	0.830	0.584	∞	input port clock
Path 5	∞	1	2	2	D_15	Q_15_reg/D	1.413	0.830	0.584	∞	input port clock
Path 6	∞	1	2	2	en_15	Q_bar_15_reg/CE	1.413	0.830	0.584	∞	input port clock

Post utilization/ area summary:

Resource	Utilization	Available	Utilization %
LUT	1	41000	0.00
FF	2	82000	0.00
IO	5	300	1.67

 

Post implementation schematic:

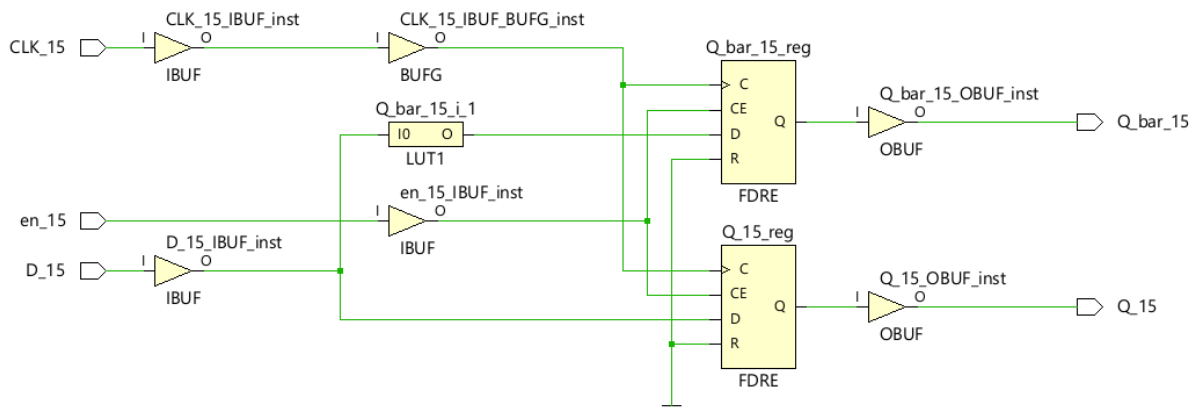


Post implementation power report:

Summary

Power estimation from Synthesized netlist. Activity derived from constraints files, simulation files or vectorless analysis. Note: these early estimates can change after implementation.

Total On-Chip Power: 0.595 W
Design Power Budget: Not Specified
Process: typical
Power Budget Margin: N/A
Junction Temperature: 26.1°C
 Thermal Margin: 58.9°C (31.1 W)
 Ambient Temperature: 25.0 °C
 Effective θ_{JA} : 1.9°C/W
 Power supplied to off-chip devices: 0 W

On-Chip Power

 


Post implementation timing summary:

Name	Slack	Levels	Routes	High Fanout	From	To	Total Delay	Logic Delay	Net Delay	Requirement	Source Clock
↳ Path 1	∞	2	2	1	Q_15_reg/C	Q_15	3.419	2.836	0.584	∞	
↳ Path 2	∞	2	2	1	Q_bar_15_reg/C	Q_bar_15	3.419	2.836	0.584	∞	
↳ Path 3	∞	2	3	2	D_15	Q_bar_15_reg/D	1.466	0.883	0.584	∞	input port clock
↳ Path 4	∞	1	2	2	en_15	Q_15_reg/CE	1.413	0.830	0.584	∞	input port clock
↳ Path 5	∞	1	2	2	D_15	Q_15_reg/D	1.413	0.830	0.584	∞	input port clock
↳ Path 6	∞	1	2	2	en_15	Q_bar_15_reg/CE	1.413	0.830	0.584	∞	input port clock

Post implementation utilization/ area summary:

Resource	Utilization	Available	Utilization %
LUT	1	41000	0.00
FF	2	82000	0.00
IO	5	300	1.67

 

Conclusion:

- In this experiment, we written Verilog code for a circuit of T flip flop, SR flip flop, D flip flop verified its output and Schematic using its test bench and we got desired output.