 


Experiment 4

Aim: Write Verilog code to create a 2x4 Decoder using Behavioural Modeling and implement a 4x16 Decoder using 2x4 Decoder.

Theory:

A 2x4 decoder is a combinational digital circuit that has two inputs (A and B) and four outputs (Y0, Y1, Y2, and Y3). It is used to select one of the four output lines based on the input values. When the input values are 00, Y0 is active, when the input is 01, Y1 is active, and so on.




Implementation 2-to-4 decoder with enable

Decimal value	Enable	Inputs		Outputs			
	E	A ₁	A ₀	D ₀	D ₁	D ₂	D ₃
	0	X	X	0	0	0	0
0	1	0	0	1	0	0	0
1	1	0	1	0	1	0	0
2	1	1	0	0	0	1	0
3	1	1	1	0	0	0	1

Truth table of 2-to-4 decoder with enable

Implementing a 4x16 Decoder Using 2x4 Decoders:

A 4x16 decoder is a digital circuit that has four inputs (D0, D1, D2, D3) and sixteen outputs (Y0 to Y15). It selects one of the sixteen output lines based on the four input lines. We can implement a 4x16 decoder using 2x4 decoders.

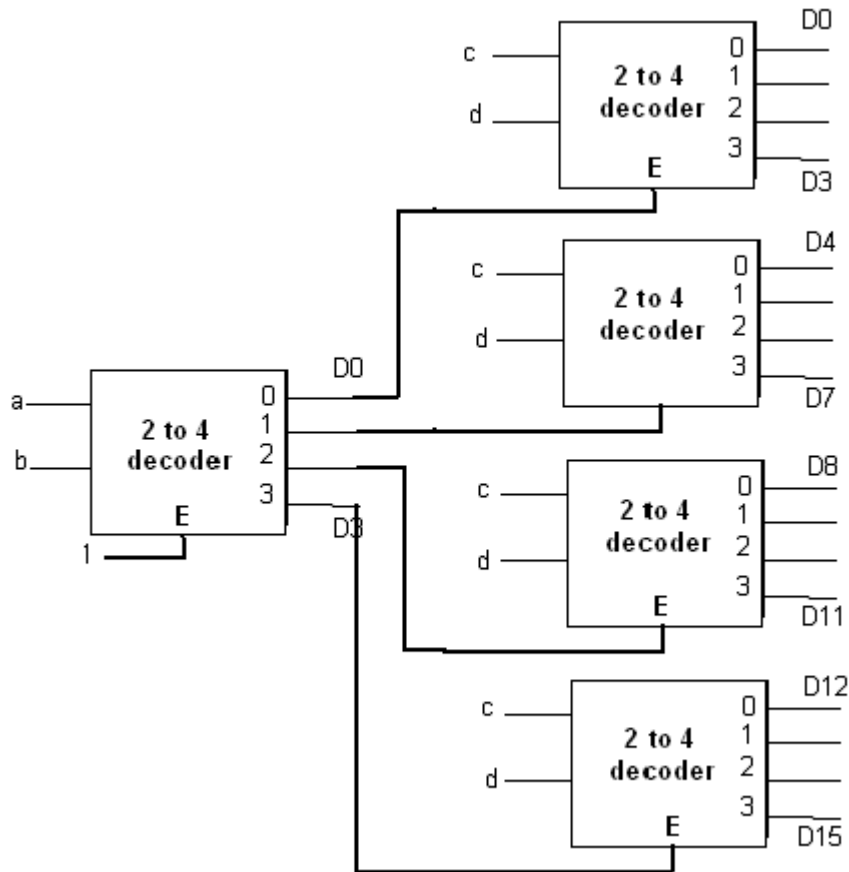Truth table of 4x16 Decoder:

D0	D1	D2	D3	Y0	Y1	Y2	Y3	Y4	Y5	Y6	Y7	Y8	Y9	Y10	Y11	Y12	Y13	Y14	Y15
0	0	0	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
0	0	0	1	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0
0	0	1	0	0	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0
0	0	1	1	0	0	0	1	0	0	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	1	0	0	0	0	0	0	0	0	0	0	0
0	1	0	1	0	0	0	0	0	1	0	0	0	0	0	0	0	0	0	0
0	1	1	0	0	0	0	0	0	0	1	0	0	0	0	0	0	0	0	0
0	1	1	1	0	0	0	0	0	0	0	1	0	0	0	0	0	0	0	0
1	0	0	0	0	0	0	0	0	0	0	0	0	1	0	0	0	0	0	0
1	0	0	1	0	0	0	0	0	0	0	0	0	0	1	0	0	0	0	0
1	0	1	0	0	0	0	0	0	0	0	0	0	0	0	1	0	0	0	0
1	0	1	1	0	0	0	0	0	0	0	0	0	0	0	0	1	0	0	0
1	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1	0	0
1	1	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1


Code:**Behavioural**

- **2x4 decoder:**


```

module decoder_2x4(en,a0,a1,y);
  input en,a0,a1;
  output reg [3:0]y;
  always @(en,a0,a1)
  begin
    if(en==1)
      begin
        if(a0==1'b0 & a1==1'b0) y=4'b0001;
        else if(a0==1'b0 & a1==1'b1) y=4'b0010;
        else if(a0==1'b1 & a1==1'b0) y=4'b0100;
        else if(a0==1'b1 & a1==1'b1) y=4'b1000;
        else y=4'bxxxx;
      end
    else
      y=4'b0000;
    end
  end
endmodule

```

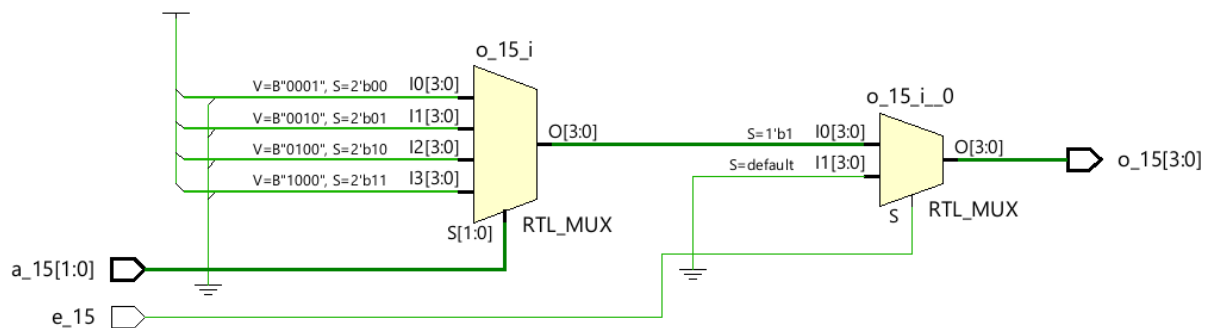RTL Schematic:

Function Verification:

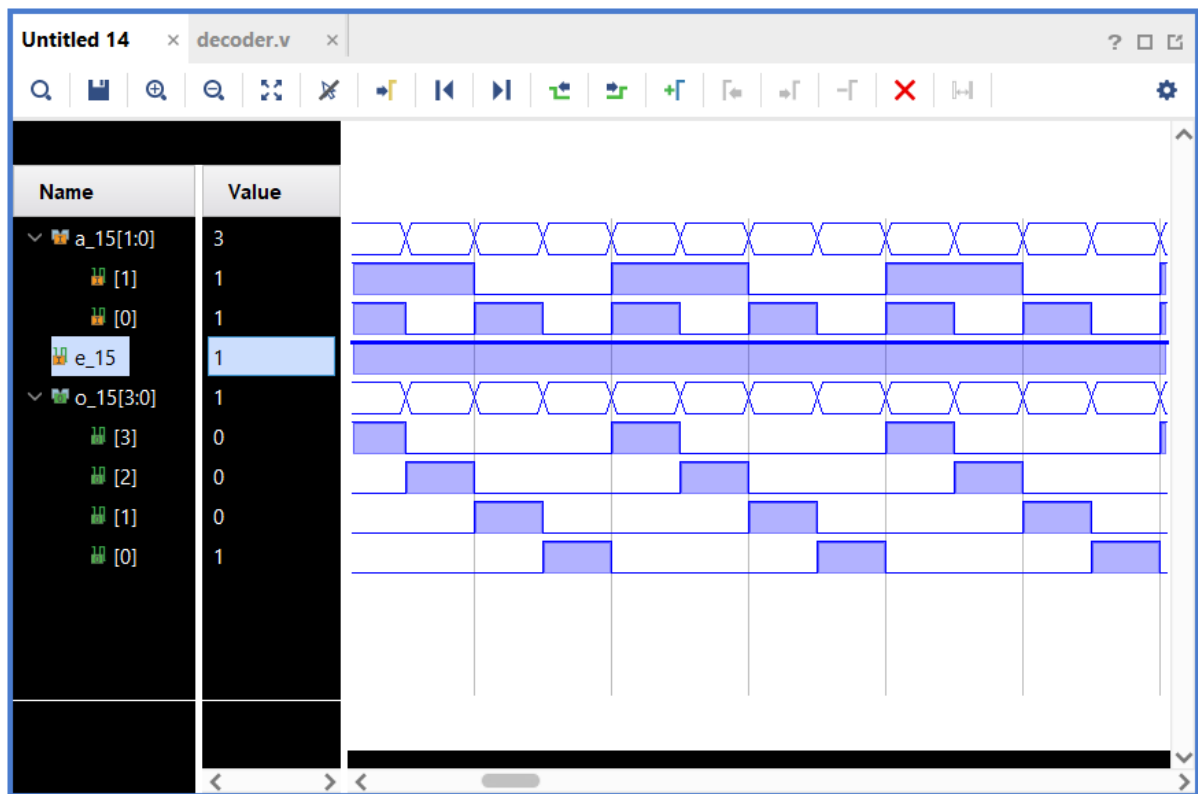


Post power report:

Summary

Power estimation from Synthesized netlist. Activity derived from constraints files, simulation files or vectorless analysis. Note: these early estimates can change after implementation.

Total On-Chip Power: 0.811 W
Design Power Budget: Not Specified
Process: typical
Power Budget Margin: N/A
Junction Temperature: 26.5°C
 Thermal Margin: 58.5°C (30.8 W)
 Ambient Temperature: 25.0 °C
 Effective θ_{JA} : 1.9°C/W
 Power supplied to off-chip devices: 0 W

On-Chip Power

 

Post synthesis timing summary:


Unconstrained Paths - NONE - NONE - Setup

Name	Slack	Levels	Routes	High Fanout	From	To	Total Delay	Logic Delay	Net Delay	Requirement	Source Clock
Path 1	∞	3	4	4	e_15	o_15[2]	4.526	3.359	1.167	∞	input port clock
Path 2	∞	3	4	4	e_15	o_15[3]	4.526	3.359	1.167	∞	input port clock
Path 3	∞	3	4	4	a_15[0]	o_15[0]	4.512	3.345	1.167	∞	input port clock
Path 4	∞	3	4	4	a_15[0]	o_15[1]	4.512	3.345	1.167	∞	input port clock


Post utilization/ area summary:

Summary

Resource	Utilization	Available	Utilization %
LUT	2	41000	0.00
IO	7	300	2.33

 

Post implementation schematic:

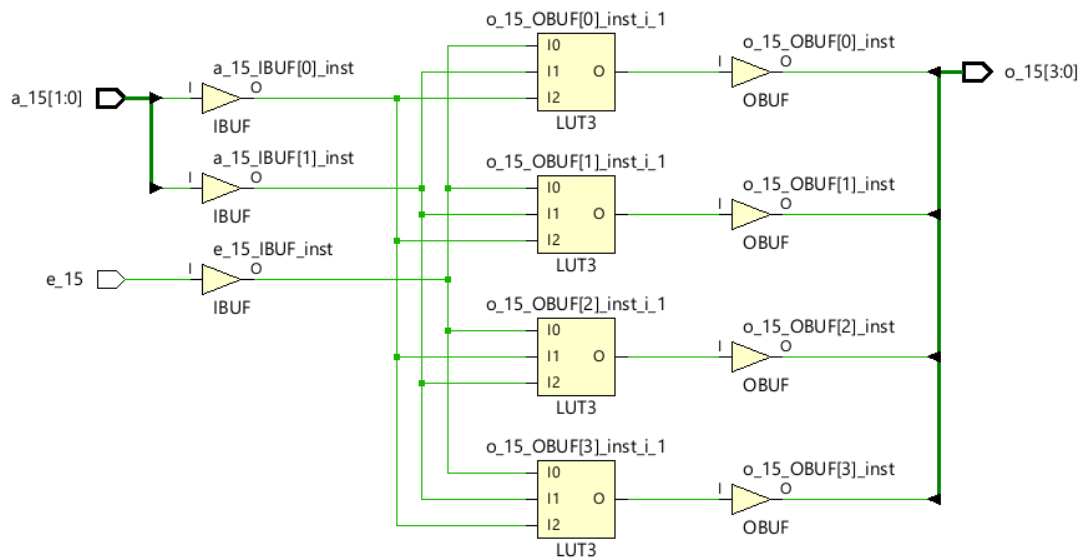


Post implementation power report:

Summary

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power: 0.747 W
Design Power Budget: Not Specified
Process: typical
Power Budget Margin: N/A
Junction Temperature: 26.4°C
 Thermal Margin: 58.6°C (30.9 W)
 Ambient Temperature: 25.0 °C
 Effective θ_{JA} : 1.9°C/W
 Power supplied to off-chip devices: 0 W

On-Chip Power

 


Post implementation timing summary:

Name	Slack	Levels	Routes	High Fanout	From	To	Total Delay	Logic Delay	Net Delay	Requirement	Source Clock
↳ Path 1	∞	3	2	4	a_15[0]	o_15[2]	6.018	3.443	2.575	∞	input port clock
↳ Path 2	∞	3	2	4	a_15[0]	o_15[1]	5.752	3.272	2.480	∞	input port clock
↳ Path 3	∞	3	2	4	e_15	o_15[3]	5.635	3.327	2.308	∞	input port clock
↳ Path 4	∞	3	2	4	e_15	o_15[0]	5.604	3.419	2.185	∞	input port clock

Post implementation utilization/ area summary:

Resource	Utilization	Available	Utilization %
LUT	2	41000	0.00
IO	7	300	2.33

 

- **4x16 decoder:**

```

module decoder2x4(
    input[1:0] a,
    input e,
    output reg [3:0] o
);
always@(*)
    if (e)
        begin
            case(a)
                2'b00:begin
                    o[0]=1'b1;
                    o[3:1]=0;
                end
                2'b01:begin
                    o[1]=1'b1;
                    o[3:2]=0;
                    o[0]=0;
                end
                2'b10:begin
                    o[2]=1'b1;
                    o[3]=0;
                    o[1:0]=0;
                end
                2'b11:begin
                    o[3]=1'b1;
                    o[2:0]=0;
                end
            default:o=0;
        end
    end

```

```
        endcase
    end
    else
        o=0;
    endmodule

module decoder4x16(
    input[3:0] a,
    output [15:0] o
);
    wire [3:0] t;
    decoder2x4 d1(.a(a[3:2]),.e(1'b1),.o(t));
    decoder2x4 d2(.a(a[1:0]),.e(t[0]),.o(o[3:0]));
    decoder2x4 d3(.a(a[1:0]),.e(t[1]),.o(o[7:4]));
    decoder2x4 d4(.a(a[1:0]),.e(t[2]),.o(o[11:8]));
    decoder2x4 d5(.a(a[1:0]),.e(t[3]),.o(o[15:12]));
endmodule
```

- **4x16 decoder Testbench:**

```
module testbench_decoder4x16;

    // Inputs
    reg [3:0] a;

    // Outputs
    wire [15:0] o;

    // Instantiate the decoder
    decoder4x16 uut (
        .a(a),
        .o(o)
    );

    // Clock signal
    reg clk = 0;
    always begin
        #5 clk = ~clk;
    end

    // Test vector
    initial begin
        $display("Testing 4x16 Decoder");
        $monitor("a = %b, o = %b", a, o);

        // Test all possible input combinations
```

```

for (a = 0; a < 16; a = a + 1) begin
    #10; // Wait for some time to observe the output
end


// Terminate the simulation
$finish;
end

endmodule


// Simulate the testbench
module tb_decoder4x16;
    reg clk;
    initial begin
        clk = 0;
        $dumpfile("decoder4x16.vcd");
        $dumpvars(0, tb_decoder4x16);
        $display("Starting simulation");
        // Simulate for 100 time units
        repeat (100) begin
            #5 clk = ~clk;
        end
    end
    $finish;
end
endmodule

```

RTL Schematic:

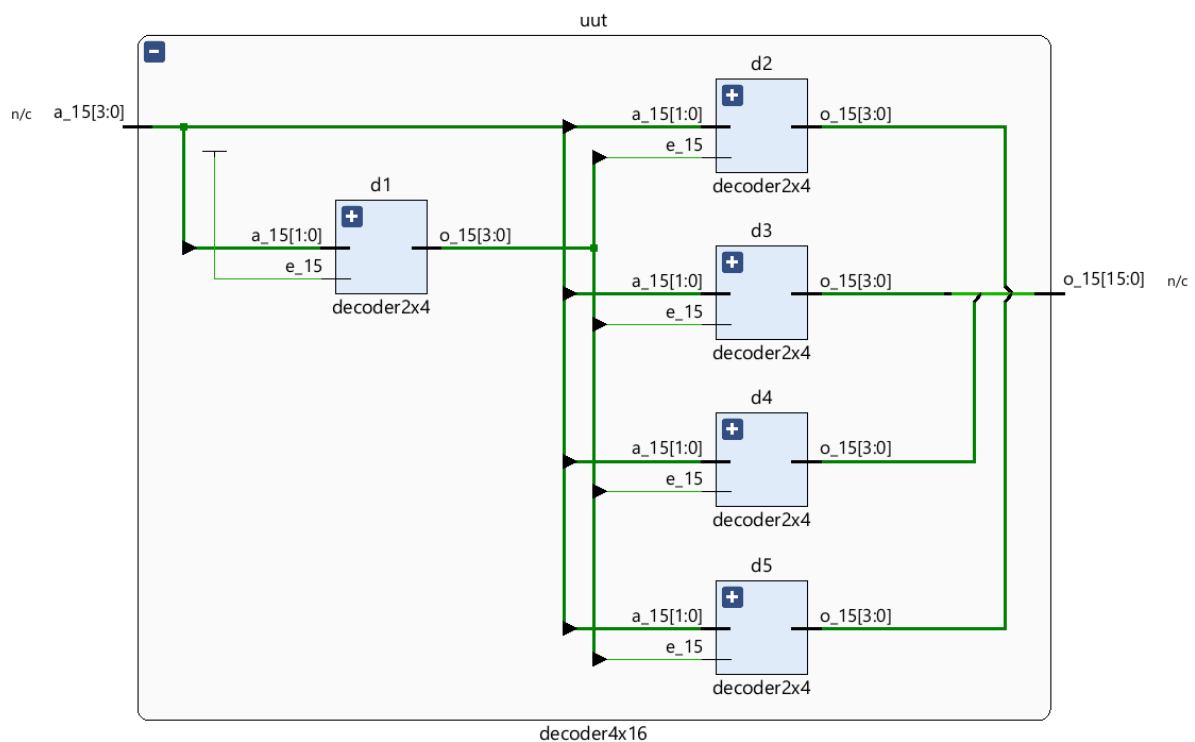

Function Verification:

 


Post power report:

Summary

Power estimation from Synthesized netlist. Activity derived from constraints files, simulation files or vectorless analysis. Note: these early estimates can change after implementation.

Total On-Chip Power: 0.079 W
Design Power Budget: Not Specified
Process: typical
Power Budget Margin: N/A
Junction Temperature: 25.1°C
 Thermal Margin: 59.9°C (31.6 W)
 Ambient Temperature: 25.0 °C
 Effective θ_{JA} : 1.9°C/W

On-Chip Power

 

Dynamic: 0.000 W (0%)
 Device Static: 0.079 W (100%)

Conclusion:

- In this experiment, we written Verilog code for 2x4 decoder and using this decoder we have implemented 4x16 decoder and verified its Schematic and outputs, area utilization and its power consumption.