

Experiment 3

Aim: Write Verilog codes for all given condition having structural, data flow and behavioural model and perform synthesis by generating different synthesis and timing waveforms.

- a) 2 x 1 mux
- b) 4 x 1 mux using 2 x 1 mux
- c) 16 x 1 mux using 4 x 1 mux

Theory:

- A Multiplexer (mux) is a combinational logic circuit that selects one of the multiple input data lines and routes it to a single output line based on the select signal.
- The 2x1 mux has two data inputs (a and b), one select input (sel), and one output (y). It selects either a or b based on the value of sel.
- The 4x1 mux uses four 2x1 muxes to select one of the four data inputs (a, b, c, d) based on the 2-bit select input (sel).
- The 16x1 mux uses four 4x1 muxes to select one of the sixteen data inputs (data) based on the 4-bit select input (sel).
- In the structural models, lower-level muxes (2x1 and 4x1) are instantiated to build higher-level muxes (4x1 and 16x1).

Code for 2x1 mux:

1) Structural

```
module mux_2x1_s(
    input I0, I1, s,
    output out
);
    wire w1, w2, w3;
    not(w1, s);
    and(w2, I0, s);
    and(w3, I1, w1);
    or(out, w2, w3);
endmodule
```

2) Data Flow

```

module mux_2x1_d(
    input I0, I1, s,
    output out
);
    wire w1, w2, w3;
    assign w1 = ~(s);
    assign w2 = I0 & s;
    assign w3 = I1 & w1;
    assign out = w2 | w3;
endmodule

```


3) Behavioural

```


module mux_2x1_b(
    input I0, I1, s,
    output out
);
    always @(I0, I1, s)
    begin
        if (s == 1'b0)
            out = I0;
        else
            out = I1;
        end
    end
endmodule

```


RTL Schematic:

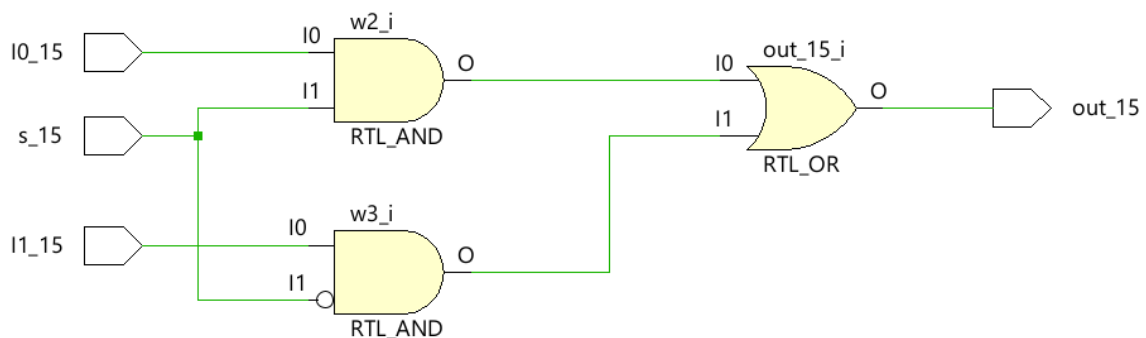

Function Verification:

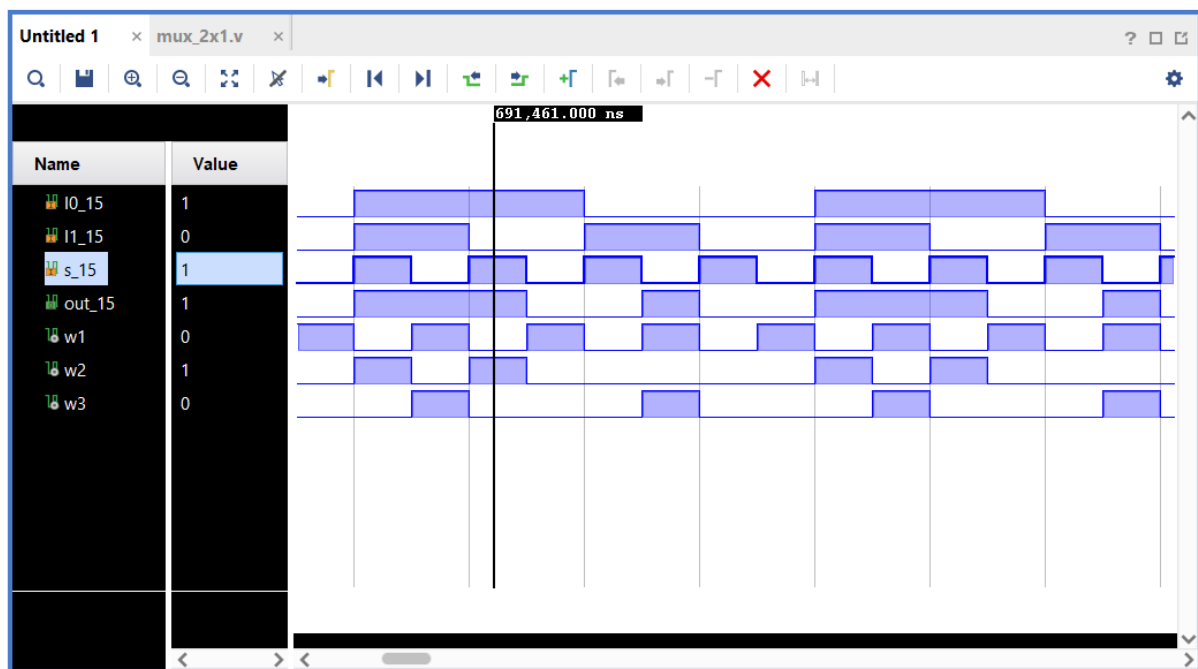

Post synthesis schematic:

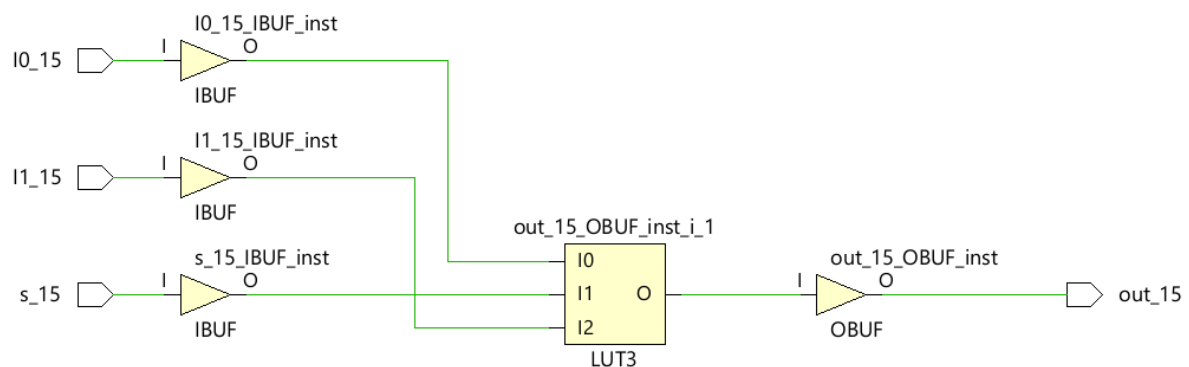


Post power report:

Summary

Power estimation from Synthesized netlist. Activity derived from constraints files, simulation files or vectorless analysis. Note: these early estimates can change after implementation.

Total On-Chip Power: 0.442 W
Design Power Budget: Not Specified
Process: typical
Power Budget Margin: N/A
Junction Temperature: 25.8°C
 Thermal Margin: 59.2°C (31.2 W)
 Ambient Temperature: 25.0 °C
 Effective θ_{JA} : 1.9°C/W
 Power supplied to off-chip devices: 0 W

On-Chip Power

 


Post synthesis timing summary:

Design Runs Timing × Power											
Unconstrained Paths - NONE - NONE - Setup											
Name	Slack ^{^1}	Levels	Routes	High Fanout	From	To	Total Delay	Logic Delay	Net Delay	Requirement	Source Clock
Path 1	∞	3	4	1	I1_15	out_15	4.512	3.345	1.167	∞	input port clock

Post utilization/ area summary:

Hierarchy			
Name ^{^1}	Slice LUTs (41000)	Bonded IOB (300)	
N mux_2x1_s	1	4	

Post implementation schematic:

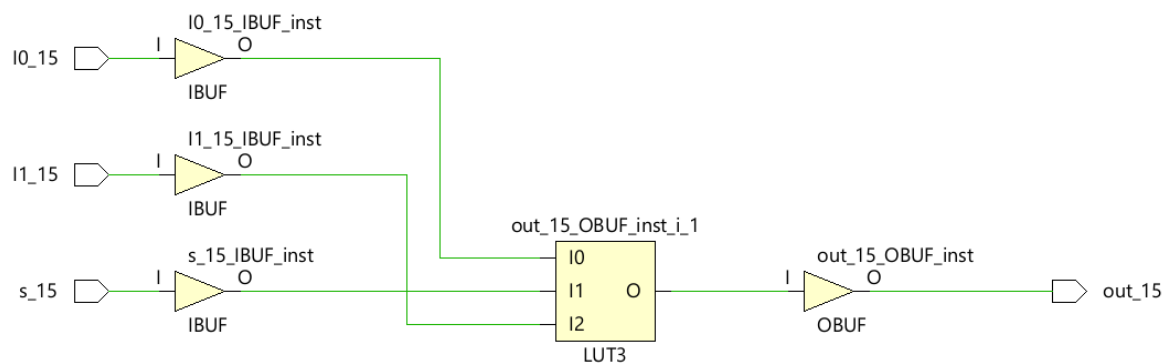


Post implementation power report:

Summary

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power:	0.435 W
Design Power Budget:	Not Specified
Process:	typical
Power Budget Margin:	N/A
Junction Temperature:	25.8°C
Thermal Margin:	59.2°C (31.2 W)
Ambient Temperature:	25.0 °C
Effective θ_{JA} :	1.9°C/W
Power supplied to off-chip devices: 0 W	

On-Chip Power

 

Post implementation timing summary:

Unconstrained Paths - NONE - NONE - Setup											
Name	Slack ^1	Levels	Routes	High Fanout	From	To	Total Delay	Logic Delay	Net Delay	Requirement	Source Clock
Path 1	∞	3	2	1	I0_15	out_15	5.615	3.274	2.341	∞	input port clock

Post implementation utilization/ area summary:

Hierarchy				
Name ^1	Slice LUTs (41000)	Slice (10250)	LUT as Logic (41000)	Bonded IOB (300)
N mux_2x1_s	1	1	1	4



Code for 4x1 mux using 2x1:**Structural**

```

module mux2x1(
    input I0, I1, s,
    output out
);
    wire w1, w2, w3;
    not(w1, s);
    and(w2, I0, s);
    and(w3, I1, w1);
    or(out, w2, w3);
endmodule

module mux_4x1(
    input I0, I1, I2, I3, s0, s1,
    output out
);
    wire w1, w2;
    mux2x1 m1(I0, I1, s0, w1);
    mux2x1 m2(I2, I3, s0, w2);
    mux2x1 m3(w1, w2, s1, out);
endmodule

```

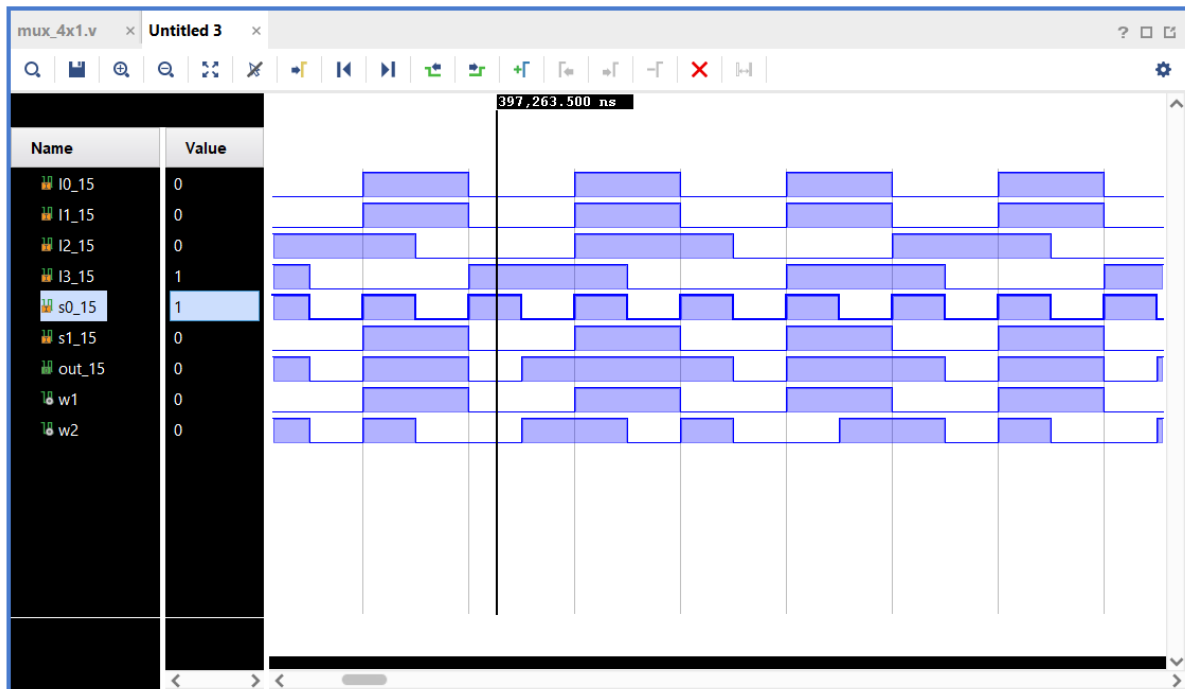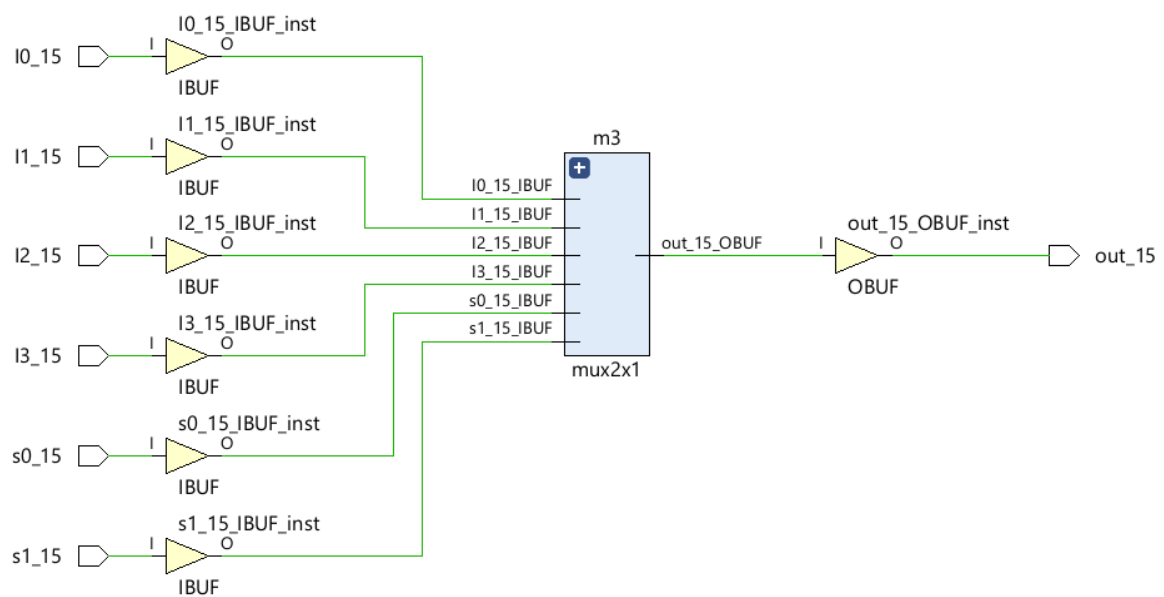RTL Schematic:**Function Verification:****Post synthesis schematic:**


Post power report:

Summary

Power estimation from Synthesized netlist. Activity derived from constraints files, simulation files or vectorless analysis. Note: these early estimates can change after implementation.

Total On-Chip Power: **0.544 W**
Design Power Budget: **Not Specified**
Process: **typical**
Power Budget Margin: **N/A**
Junction Temperature: **26.0°C**
 Thermal Margin: 59.0°C (31.1 W)
 Ambient Temperature: 25.0 °C
 Effective θ_{JA} : 1.9°C/W

On-Chip Power

 

Post synthesis timing summary:


Unconstrained Paths - NONE - NONE - Setup

Name	Slack	Levels	Routes	High Fanout	From	To	Total Delay	Logic Delay	Net Delay	Requirement	Source Clock
Path 1	∞	3	4	1	I3_15	out_15	4.512	3.345	1.167	∞	input port clock

Post utilization/ area summary:

Name	Slice LUTs (41000)	Bonded IOB (300)
mux_4x1	1	7
m3 (mux2x1)	1	0

Post implementation schematic:

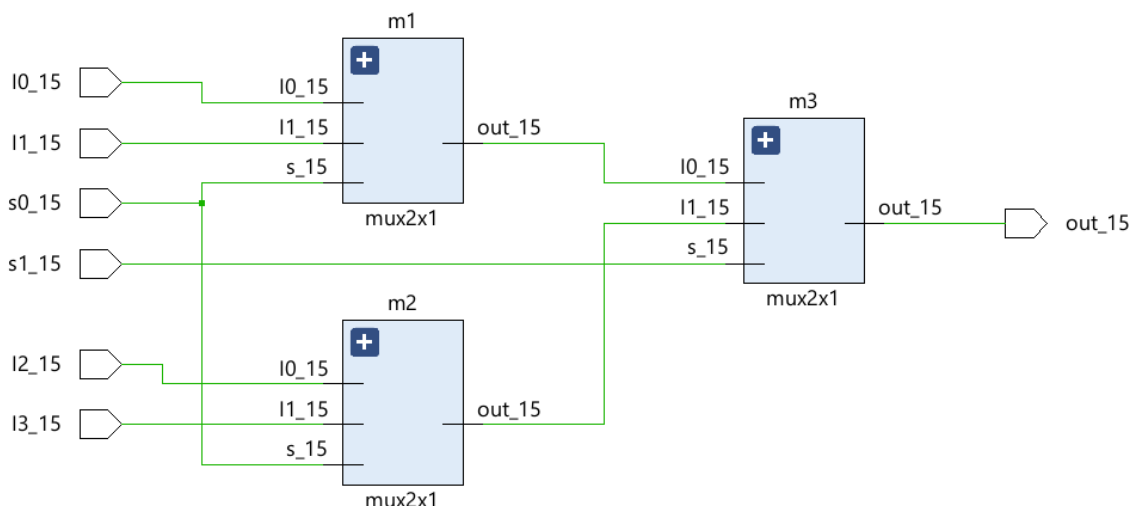


Post implementation power report:

Summary

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power: **0.535 W**
Design Power Budget: **Not Specified**
Process: **typical**
Power Budget Margin: **N/A**
Junction Temperature: **26.0°C**
 Thermal Margin: 59.0°C (31.1 W)
 Ambient Temperature: 25.0 °C

On-Chip Power

 

Post implementation timing summary:

Unconstrained Paths - NONE - NONE - Setup											
Name	Slack	Levels	Routes	High Fanout	From	To	Total Delay	Logic Delay	Net Delay	Requirement	Source Clock
Path 1	∞	3	2	1	IO_15	out_15	5.696	3.315	2.381	∞	input port clock

Post implementation utilization/ area summary:

Hierarchy				
Name	Slice LUTs (41000)	Slice (10250)	LUT as Logic (41000)	Bonded IOB (300)
mux_4x1	1	1	1	7
m3 (mux2x1)	1	1	1	0

Code for 16x1 mux using 4x1 mux:

Structural

```

module m_2x1(
    input I0, I1,
    input sel,
    output out
);
    assign out = (sel) ? I1 : I0;
endmodule

module m_4x1(
    input [3:0] I0, I1, I2, I3,
    input [1:0] sel,
    output out

```



```
);  
wire w0, w1, w2;  
m_2x1 mux1(I0, I1, sel[0], w0);  
m_2x1 mux2(I2, I3, sel[0], w1);  
m_2x1 mux3(w0, w1, sel[1], w2);  
assign out = w2;  
endmodule  
  
module mux_16x1(data, sel, y);  
    input [15:0] data;  
    input [3:0] sel;  
    output y;  
    wire [0:3] ma;  
    m_4x1 mux1(data[3:0],sel[1:0],ma[0]);  
    m_4x1 mux2(data[7:4],sel[1:0],ma[1]);  
    m_4x1 mux3(data[11:8],sel[1:0],ma[2]);  
    m_4x1 mux4(data[15:12],sel[1:0],ma[3]);  
    m_4x1 mux5(ma,sel[3:2],y);  
endmodule
```

Test-bench

```
module tb_mux_16x1;  
  
    // Inputs and outputs of the mux_16x1 module  
    reg [15:0] data;  
    reg [3:0] sel;  
    wire y;  
  
    // Instantiate the mux_16x1 module  
    mux_16x1 u_mux (  
        .data(data),  
        .sel(sel),  
        .y(y)  
    );  
  
    // Stimulus generation without a clock  
    initial begin  
        // Initialize inputs  
        data = 16'b0000000000000000;  
        sel = 4'b0000;  
  
        // Test Case 1: Select input 0  
        data = 16'b0000000000000001;  
        sel = 4'b0000;  
        #10; // Delay for simulation purposes
```

```
// Test Case 2: Select input 1
data = 16'b0000000000000010;
sel = 4'b0001;
#10; // Delay for simulation purposes
```

```
// Test Case 3: Select input 2
data = 16'b0000000000000100;
sel = 4'b0010;
#10; // Delay for simulation purposes
```

```
// Test Case 4: Select input 3
data = 16'b0000000000001000;
sel = 4'b0011;
#10; // Delay for simulation purposes
```

```
// Test Case 5: Select input 4
data = 16'b0000000000010000;
sel = 4'b0100;
#10; // Delay for simulation purposes
```

```
// Test Case 6: Select input 5
data = 16'b0000000000100000;
sel = 4'b0101;
#10; // Delay for simulation purposes
```

```
// Test Case 7: Select input 6
data = 16'b0000000001000000;
sel = 4'b0110;
#10; // Delay for simulation purposes
```

```
// Test Case 8: Select input 7
data = 16'b0000000010000000;
sel = 4'b0111;
#10; // Delay for simulation purposes
```

```
// Test Case 9: Select input 8
data = 16'b0000000100000000;
sel = 4'b1000;
#10; // Delay for simulation purposes
```

```
// Test Case 10: Select input 9
data = 16'b0000001000000000;
sel = 4'b1001;
#10; // Delay for simulation purposes
```

```
// Test Case 11: Select input 10
```

```
data = 16'b0000010000000000;
sel = 4'b1010;
#10; // Delay for simulation purposes

// Test Case 12: Select input 11
data = 16'b0000100000000000;
sel = 4'b1011;
#10; // Delay for simulation purposes

// Test Case 13: Select input 12
data = 16'b0001000000000000;
sel = 4'b1100;
#10; // Delay for simulation purposes

// Test Case 14: Select input 13
data = 16'b0010000000000000;
sel = 4'b1101;
#10; // Delay for simulation purposes



// Test Case 15: Select input 14
data = 16'b0100000000000000;
sel = 4'b1110;
#10; // Delay for simulation purposes

// Test Case 16: Select input 15
data = 16'b1000000000000000;
sel = 4'b1111;
#10; // Delay for simulation purposes


// End simulation
$finish;
end

// Display output
always @(y) begin
    $display("Output y = %b", y);
end

endmodule
```

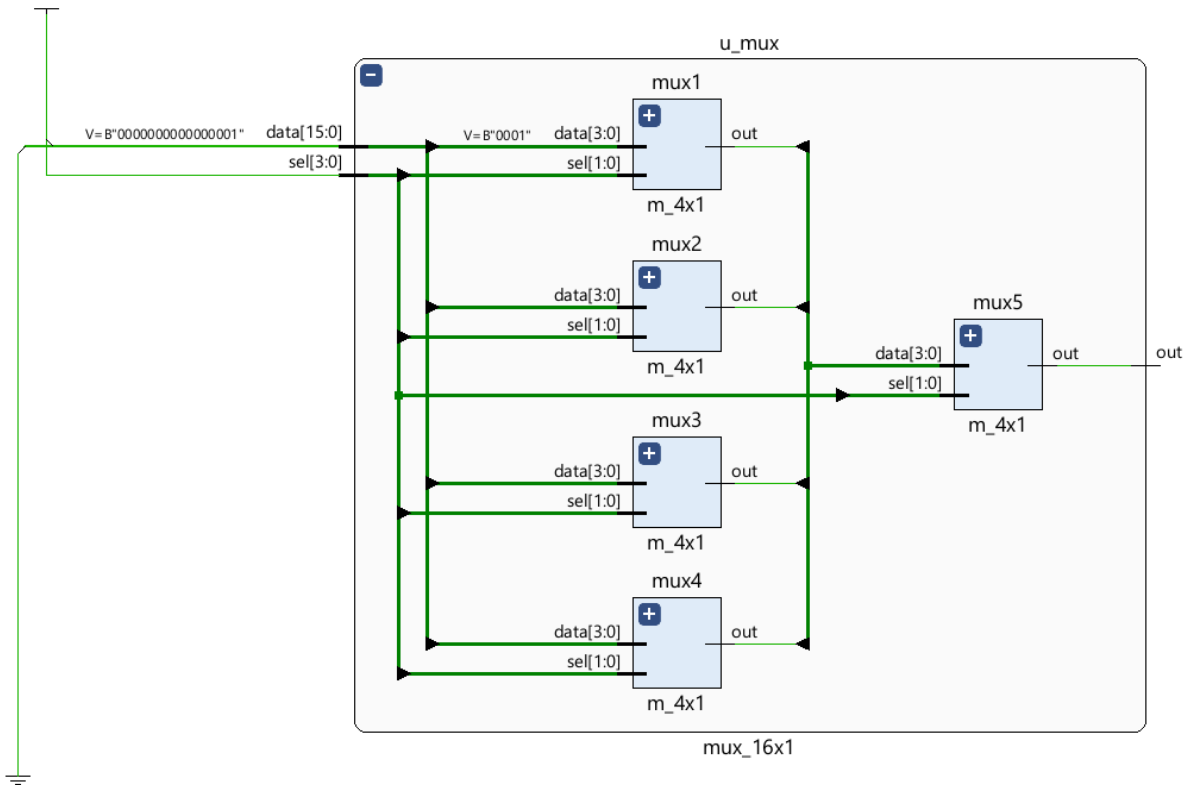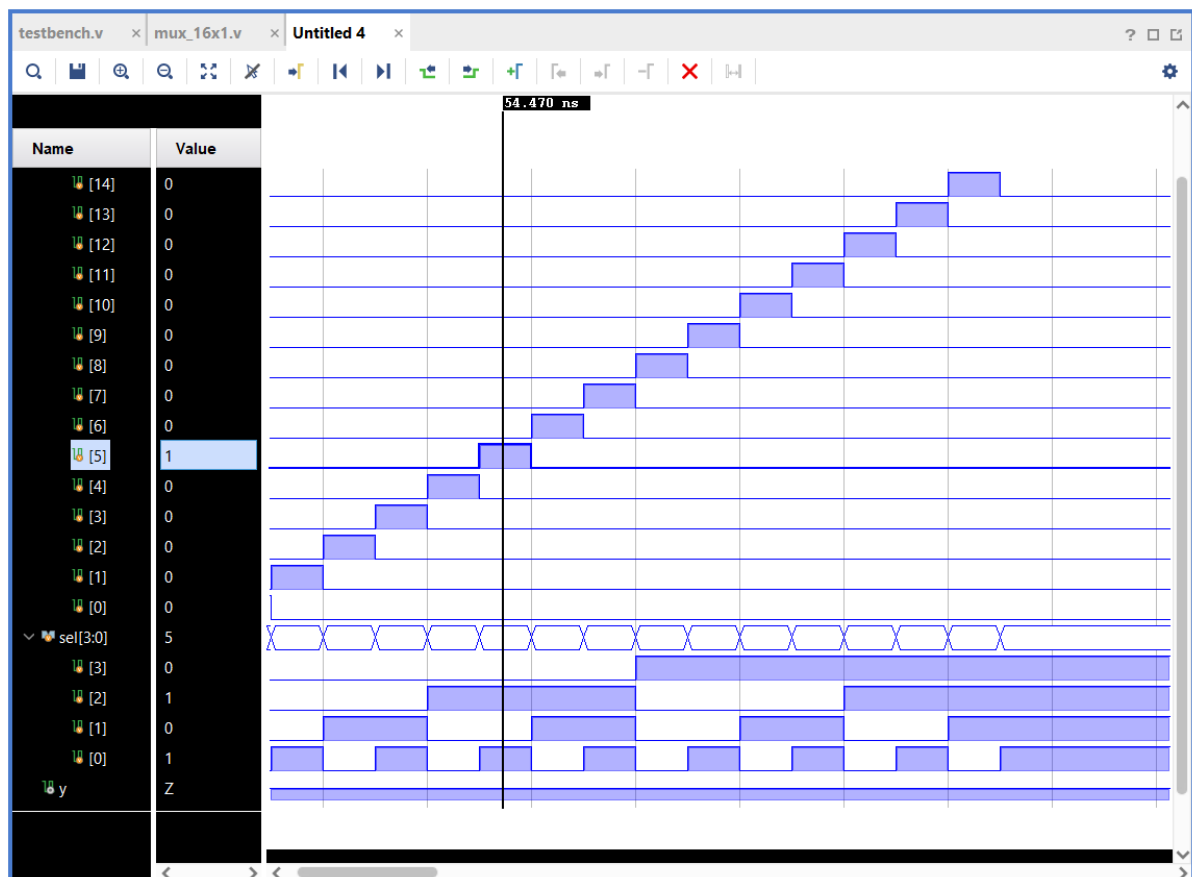RTL Schematic:**Function Verification:**

Post synthesis schematic:

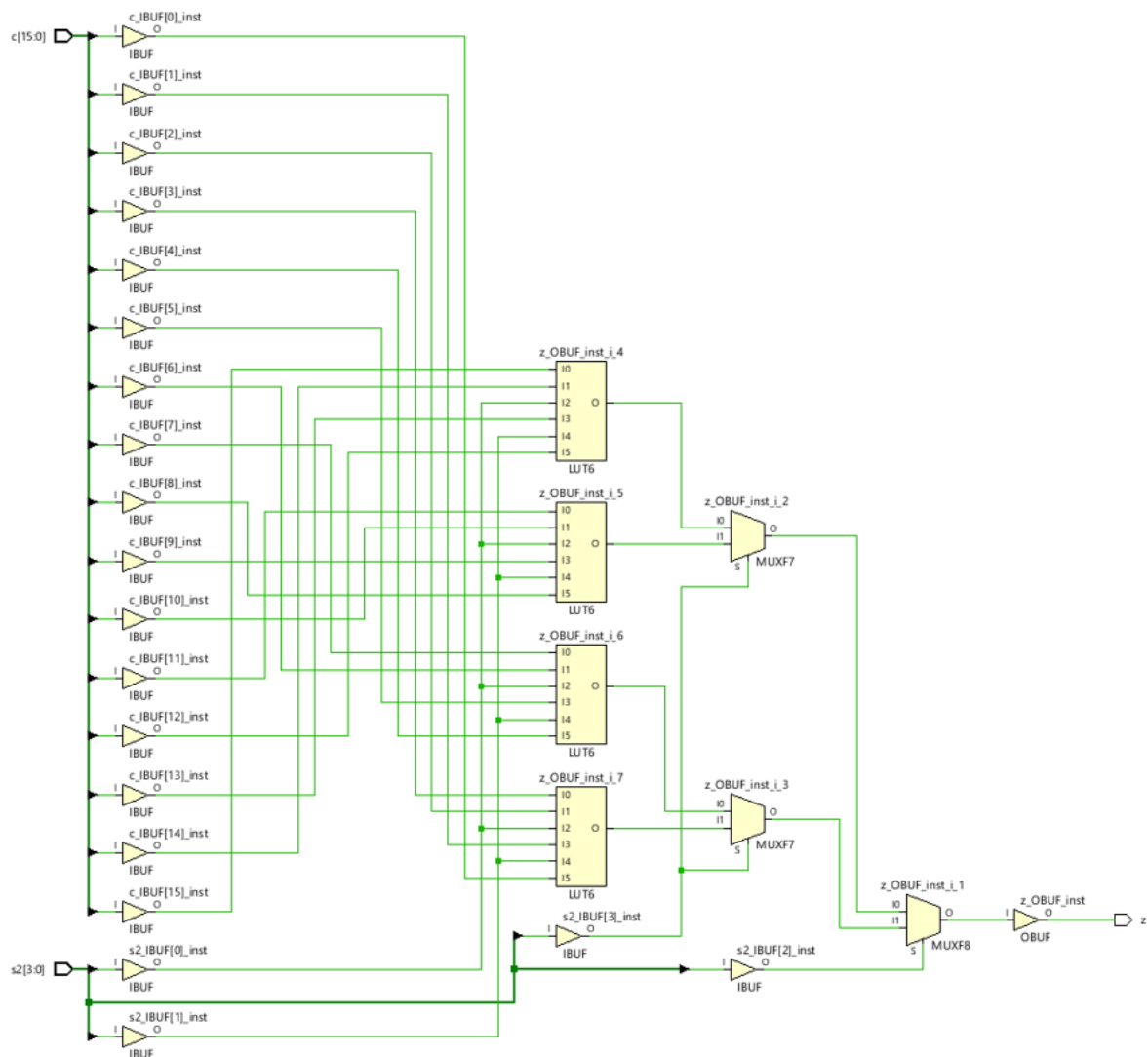


Post power report:

Summary

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power: 0.787 W
Design Power Budget: Not Specified
Process: typical
Power Budget Margin: N/A
Junction Temperature: 26.5°C
Thermal Margin: 58.5°C (30.9 W)

On-Chip Power

 

Post synthesis timing summary:

Setup	Hold	Pulse Width
Worst Negative Slack (WNS): inf	Worst Hold Slack (WHS): inf	Worst Pulse Width Slack (WPWS): NA
Total Negative Slack (TNS): 0.000 ns	Total Hold Slack (THS): 0.000 ns	Total Pulse Width Negative Slack (TPWS): NA
Number of Failing Endpoints: 0	Number of Failing Endpoints: 0	Number of Failing Endpoints: NA
Total Number of Endpoints: 1	Total Number of Endpoints: 1	Total Number of Endpoints: NA

There are no user specified timing constraints.

Post utilization/ area summary:

    Hierarchy						
Name	Slice LUTs (41000)	F7 Muxes (20500)	F8 Muxes (10250)	Slice (10250)	LUT as Logic (41000)	Bonded IOB (300)
N mux161	4	2	1	1	4	21