

Experiment 1

Aim: Write Verilog codes for all basic logic gates having structural, data flow and behavioural model and perform synthesis by generating different synthesis and timing waveforms.

Theory:7

Basic Logic Gates

There are seven fundamental types of logic gates: AND, OR, XOR, NAND, NOR, XNOR, and NOT. These essential digital devices operate based on Boolean functions and are employed to perform logical operations on single or multiple binary inputs, resulting in a single binary output.

(1) OR Gate:

The OR gate produces an output of 1 if at least one of its inputs is set to 1. Its Boolean expression is represented as:

$$Y = A \text{ OR } B$$

(2) AND Gate:

An AND gate generates an output of 1 only when all of its inputs are set to 1. Its Boolean expression is:

$$Y = A \text{ AND } B$$

(3) NAND Gate:

The NAND gate is a digital circuit with two or more inputs that outputs the logical AND of all those inputs, but inverted. Its expression is:

$$Y = \text{NOT } (A \text{ AND } B)$$

(4) NOR Gate:

A NOR gate, with two or more inputs, produces an output that is the logical OR of all those inputs, but inverted:

$$Y = \text{NOT } (A \text{ OR } B)$$

(5) XOR Gate:

Known as the Exclusive-OR gate, the XOR gate outputs 1 when the number of true inputs is odd. Its expression is:

$$Y = A \text{ XOR } B$$

(6) XNOR Gate:

The XNOR gate is the logical complement of the XOR gate, producing an output of 1 when the inputs are equal. Its expression is:

$$Y = \text{NOT } (A \text{ XOR } B)$$

Code:**1) Structural**



```
module basicgate_s(  
    input a, b,  
    output c  
);  
    and(and, a, b);  
    or(or, a, b);  
    nand(nand, a, b);  
    nor(nor, a, b);  
    xor(xor, a, b);  
    xnor(xnor, a, b);  
endmodule
```

2) Data Flow


```
module basicgate_d(  
    input a, b,  
    output c  
);  
    assign and = a & b;  
    assign or = a | b;  
    assign nand = ~(a & b);  
    assign nor = ~(a | b);  
    assign xor = a ^ b;  
    assign xnor = ~(a ^ b);  
endmodule
```

3) Behavioural

```
module basicgate_b(  
    input a, b,  
    output reg and, or, nand, nor, xor, xnor  
);  
    always @(a, b)  
    begin  
        and = a & b;  
        or = a | b;  
        nand = ~(a & b);  
        nor = ~(a | b);  
        xor = a ^ b;  
        xnor = ~(a ^ b);  
    end  
endmodule
```

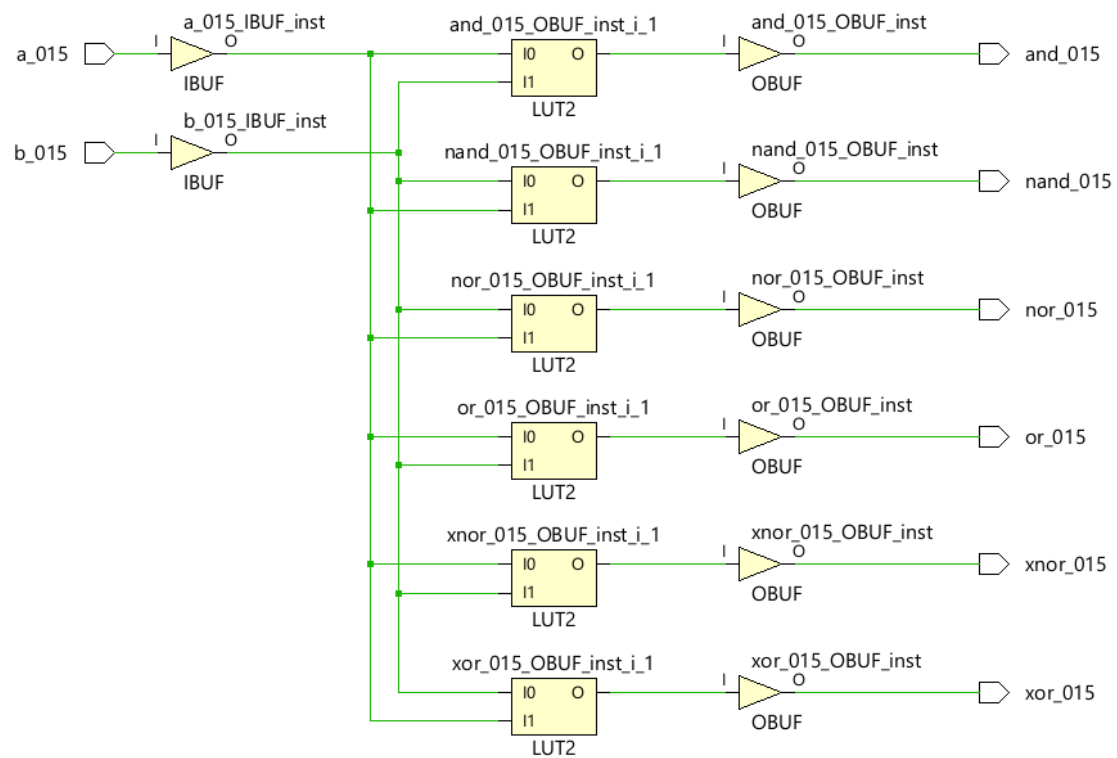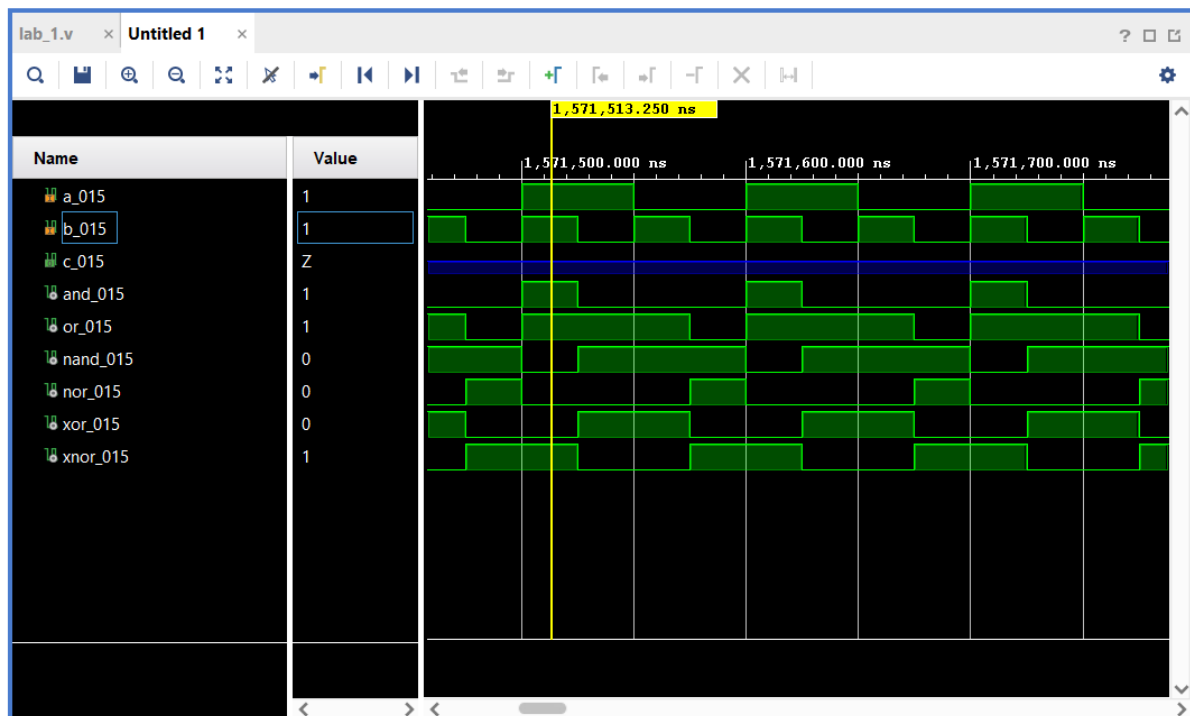RTL Schematic:**Function Verification:**

Post synthesis schematic:

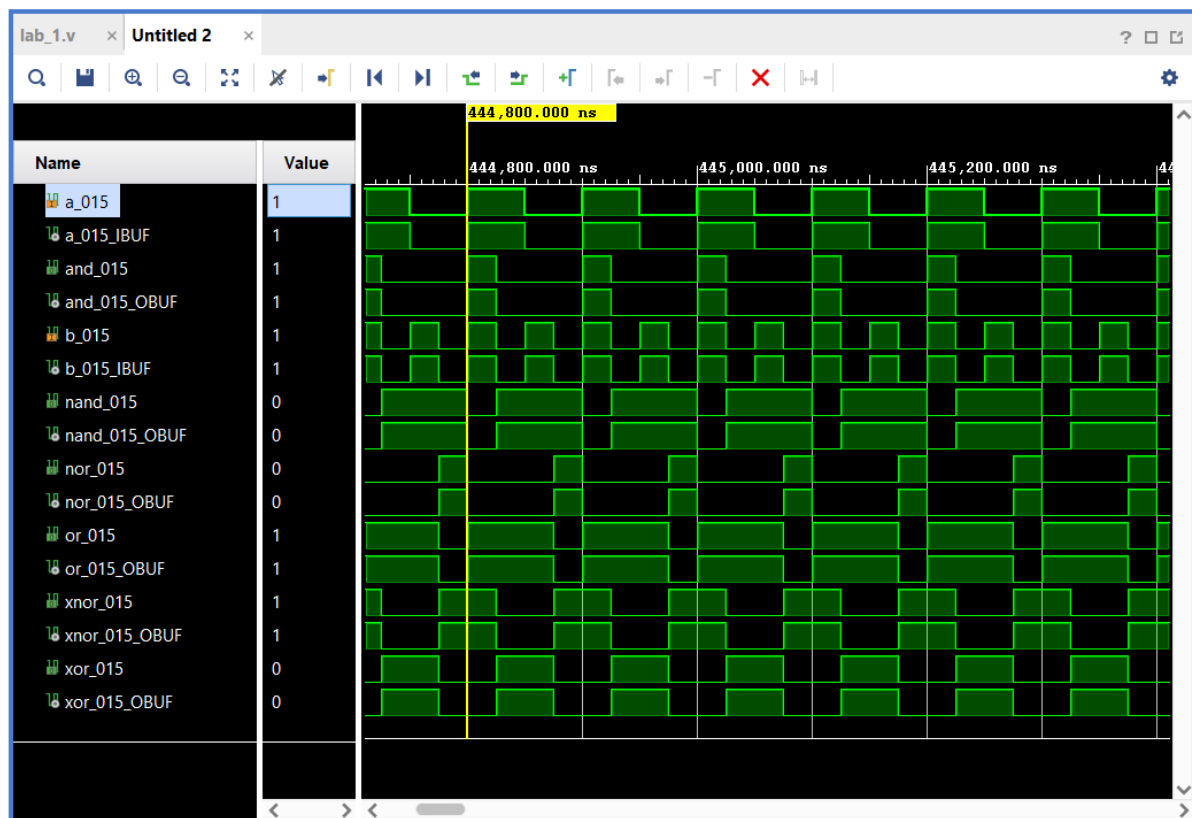


Post power report:

Summary

Power estimation from Synthesized netlist. Activity derived from constraints files, simulation files or vectorless analysis. Note: these early estimates can change after implementation.

Total On-Chip Power:	1.883 W
Design Power Budget:	Not Specified
Process:	typical
Power Budget Margin:	N/A
Junction Temperature:	28.5°C
Thermal Margin:	56.5°C (29.8 W)
Ambient Temperature:	25.0 °C
Effective θ_{JA} :	1.9°C/W
Power supplied to off-chip devices:	0 W
Confidence level:	Low

On-Chip Power

 

Post synthesis timing summary:

Design Timing Summary


Setup	Hold	Pulse Width
Worst Negative Slack (WNS): inf	Worst Hold Slack (WHS): inf	Worst Pulse Width Slack (WPWS): NA
Total Negative Slack (TNS): 0.000 ns	Total Hold Slack (THS): 0.000 ns	Total Pulse Width Negative Slack (TPWS): NA
Number of Failing Endpoints: 0	Number of Failing Endpoints: 0	Number of Failing Endpoints: NA
Total Number of Endpoints: 6	Total Number of Endpoints: 6	Total Number of Endpoints: NA

There are no user specified timing constraints.

Post utilization/ area summary:

Reports	Design Runs	Utilization	Timing	Power
Hierarchy				
Name	Slice LUTs (41000)	Bonded IOB (300)		
basicgate_s	3	8		

Post implementation schematic:

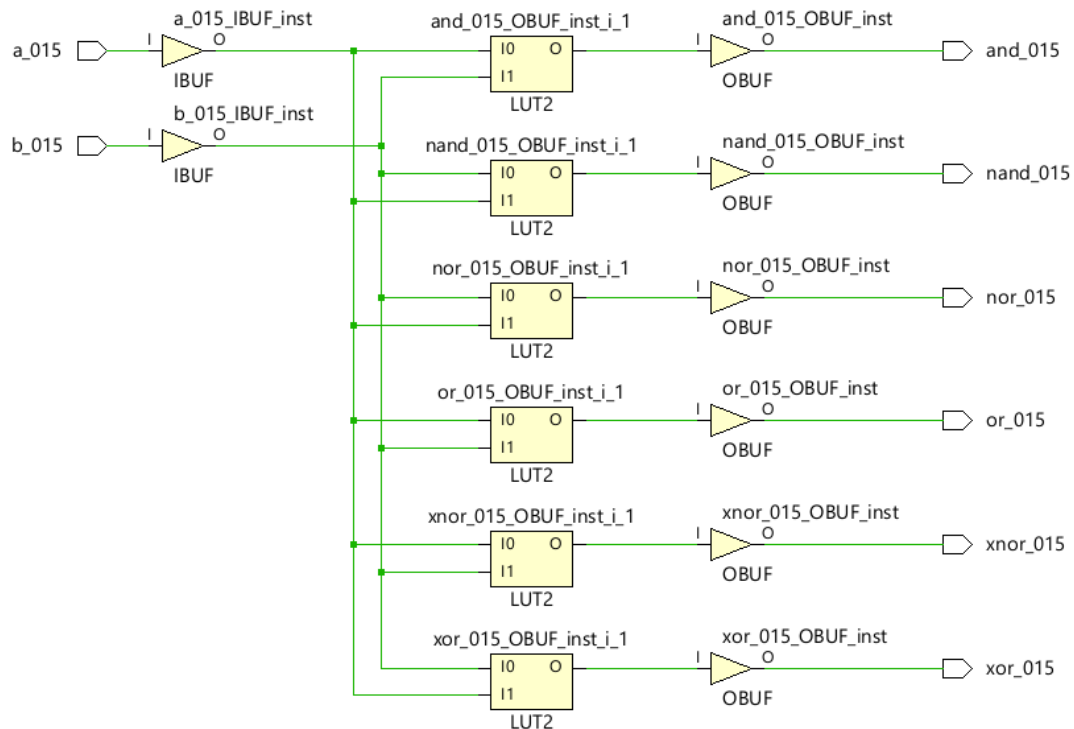


Post implementation power report:

Summary

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power: 1.855 W
Design Power Budget: Not Specified
Process: typical
Power Budget Margin: N/A
Junction Temperature: 28.5°C
 Thermal Margin: 56.5°C (29.8 W)
 Ambient Temperature: 25.0 °C
 Effective θ_{JA} : 1.9°C/W
 Power supplied to off-chip devices: 0 W
 Confidence level: Low
[Launch Power Constraint Advisor](#) to find and fix

On-Chip Power

 

Post implementation timing summary:

Design Timing Summary

Setup	Hold	Pulse Width
Worst Negative Slack (WNS): inf	Worst Hold Slack (WHS): inf	Worst Pulse Width Slack (WPWS): NA
Total Negative Slack (TNS): 0.000 ns	Total Hold Slack (THS): 0.000 ns	Total Pulse Width Negative Slack (TPWS): NA
Number of Failing Endpoints: 0	Number of Failing Endpoints: 0	Number of Failing Endpoints: NA
Total Number of Endpoints: 6	Total Number of Endpoints: 6	Total Number of Endpoints: NA

There are no user specified timing constraints.

Post implementation utilization/ area summary:

Reports	Design Runs	DRC	Power	Timing	Utilization	×
<div> <div>Q</div> <div>≡</div> <div>≡</div> <div>%</div> <div>Hierarchy</div> </div>						
Name	Slice LUTs (41000)	Slice (10250)	LUT as Logic (41000)	Bonded IOB (300)		
N basicgate_s	3	1	3	8		