

Experiment 2

Aim:

- a) Write Verilog codes for implementing **half-adder** having structural, data flow and behavioural model and perform synthesis by generating different synthesis and timing waveforms.
- b) Write Verilog codes for implementing **full-adder using half-adder** having structural, data flow and behavioural model and perform synthesis by generating different synthesis and timing waveforms.

Theory:

Half Adder:

A half adder is a digital circuit that performs binary addition of two inputs (A and B), generating a sum (S) and a carry (Cout).

A	B	Sum (S)	Carry (Cout)
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Full Adder:

A full adder is a digital circuit that performs binary addition of three inputs (A, B, and Cin), generating a sum (S) and a carry out (Cout).

Truth Table:

A	B	Cin	Sum (S)	Carry Out (Cout)
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Code for Half-adder:**1) Structural**

```

module halfAdder_s(
    input a, b,
    output c, s
);
    and(c,a,b);
    xor(s,a,b);
endmodule

```

2) Data Flow

```

module halfAdder_d(
    input a, b,
    output c, s
);
    assign c = a & b;
    assign s = a^b;
endmodule


```

3) Behavioural


```

module halfAdder_b(
    input a, b,
    output reg c, s
);
    always @(a, b)
    begin
        c = a & b;
        s = a ^ b;
    end
endmodule

```

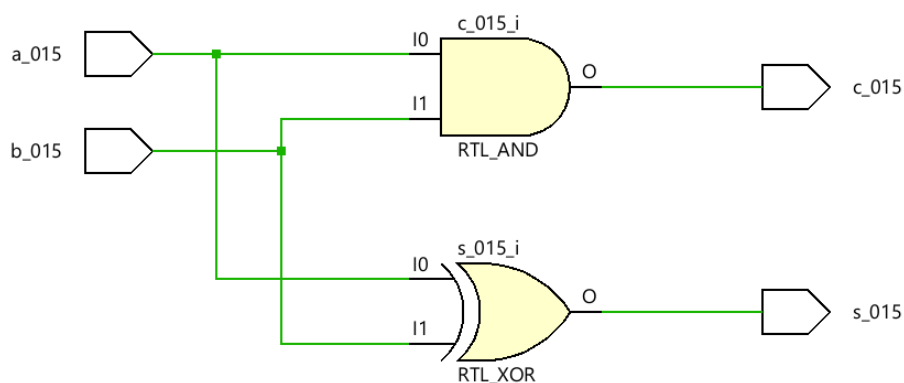RTL Schematic:

Function Verification:

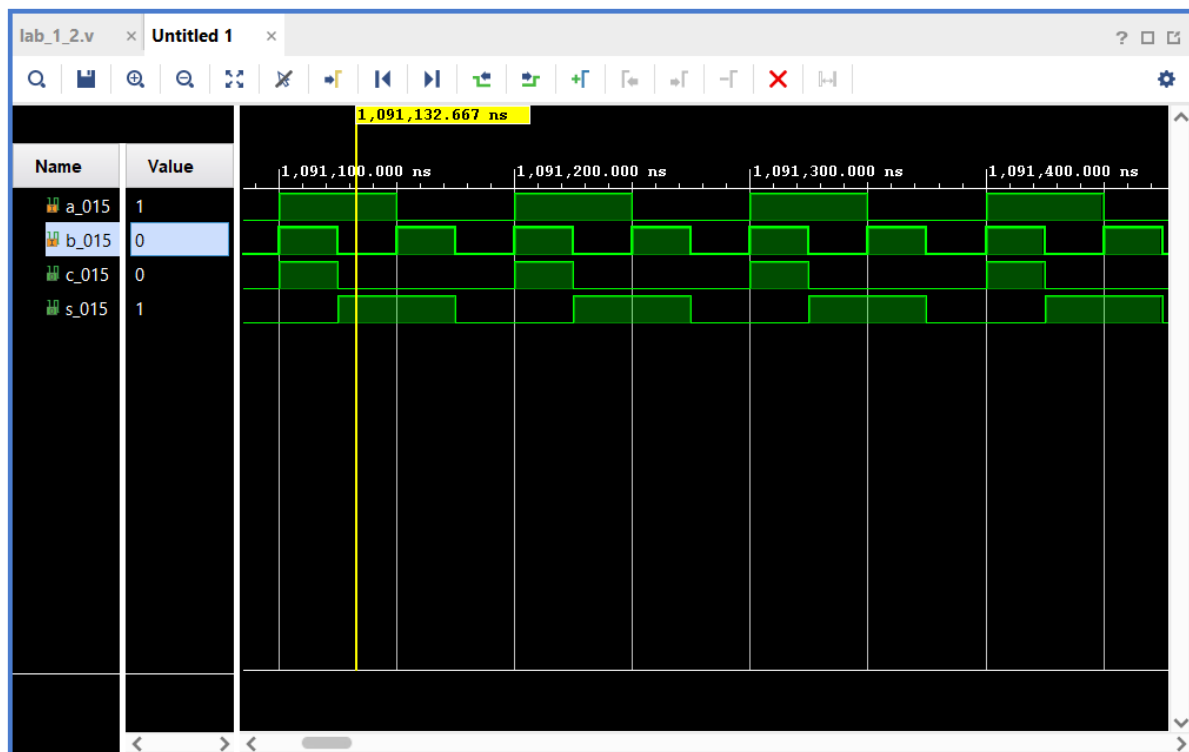


Post power report:


Summary

Power estimation from Synthesized netlist. Activity derived from constraints files, simulation files or vectorless analysis. Note: these early estimates can change after implementation.

Total On-Chip Power:	1.883 W
Design Power Budget:	Not Specified
Process:	typical
Power Budget Margin:	N/A
Junction Temperature:	28.5°C
Thermal Margin:	56.5°C (29.8 W)
Ambient Temperature:	25.0 °C
Effective θ_{JA} :	1.9°C/W
Power supplied to off-chip devices:	0 W
Confidence level:	Low


On-Chip Power

 

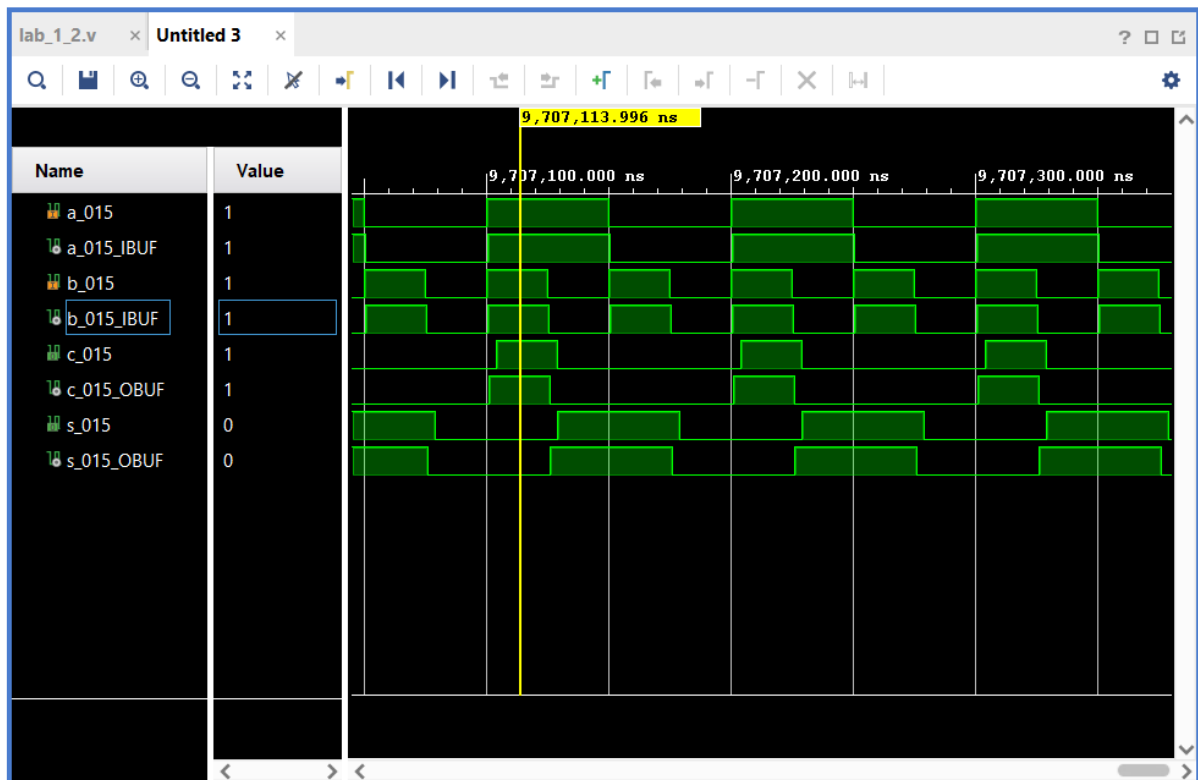Post synthesis timing summary:**Post utilization/ area summary:**

Reports	Design Runs	Utilization	Timing
Hierarchy			
Name	1	Slice LUTs (41000)	Bonded IOB (300)
halfAdder	1	1	4

Post implementation schematic:

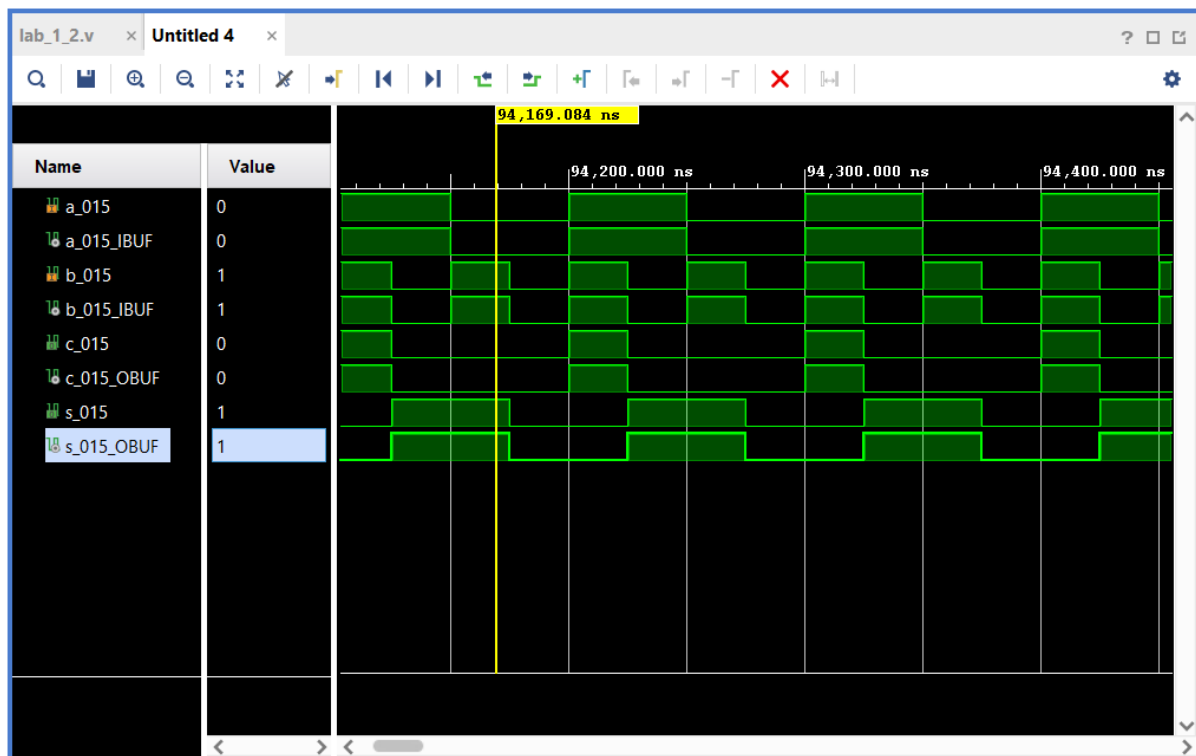


Post implementation power report:

Summary

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power: 0.744 W
Design Power Budget: Not Specified
Process: typical
Power Budget Margin: N/A
Junction Temperature: 26.4°C
 Thermal Margin: 58.6°C (30.9 W)
 Ambient Temperature: 25.0 °C
 Effective θ_{JA} : 1.9°C/W
 Power supplied to off-chip devices: 0 W
 Confidence level: Low


On-Chip Power

 

Post implementation utilization/ area summary:

Summary

Resource	Utilization	Available	Utilization %
LUT	1	41000	0.00
IO	4	300	1.33

 

Code for Full adder using Half-adder:**1) Structural**

```
module halfadder_s(  
    input a, b,  
    output c, s  
);  
    and(c,a,b);  
    xor(s,a,b);  
endmodule  
  
module full_half_s(  
    input a, b, c,  
    output sum, carry  
);  
    wire w1, w2, w3;  
    halfadder h1(.a(a), .b(b), .c(w2), .s(w1));  
    halfadder h2(.a(w1), .b(c), .c(w3), .s(sum));  
    or(carry, w2, w3);  
endmodule
```

2) Data Flow

```
module halfadder_d(  
    input a, b,  
    output c, s  
);  
    assign {c, s} = a + b;  
endmodule  
  
module full_half_d(  
    input a, b, c,  
    output sum, carry  
);  
    wire w1, w2, w3;  
    halfadder h1(.a(a), .b(b), .c(w2), .s(w1));  
    halfadder h2(.a(w1), .b(c), .c(w3), .s(sum));  
    or(carry, w2, w3);  
endmodule
```

3) Behavioural

```

module halfadder_b(
    input a, b,
    output reg c, s
);
    always @(a, b)
    begin
        c = a & b;
        s = a ^ b;
    end
endmodule


```



```

module full_half_b(
    input a, b, c,
    output sum, carry
);
    wire w1, w2, w3;
    halfadder h1(.a(a), .b(b), .c(w2), .s(w1));
    halfadder h2(.a(w1), .b(c), .c(w3), .s(sum));
    or(carry, w2, w3);
endmodule

```

RTL Schematic:

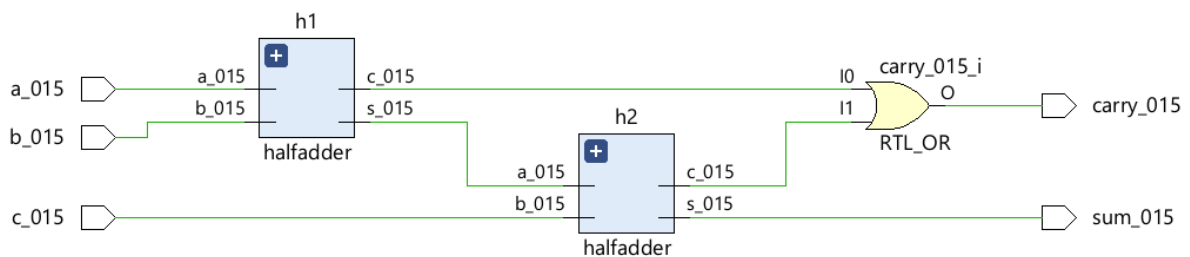

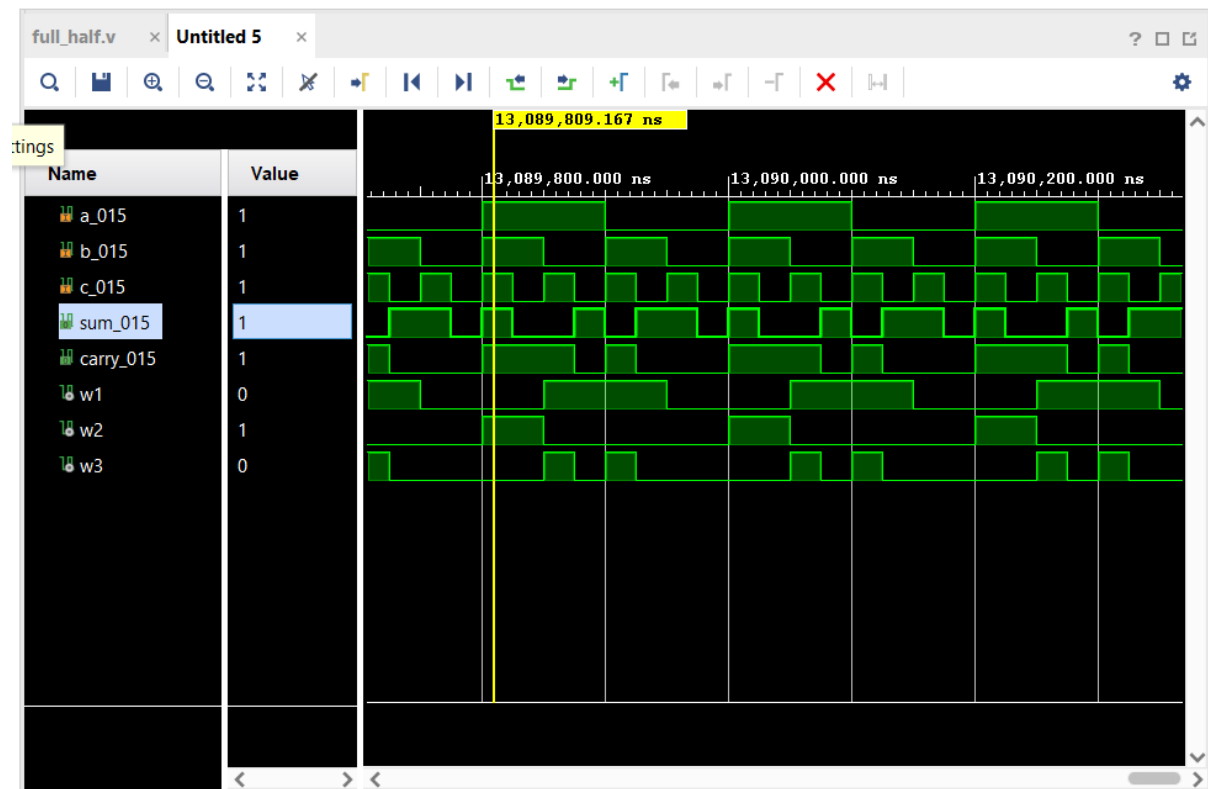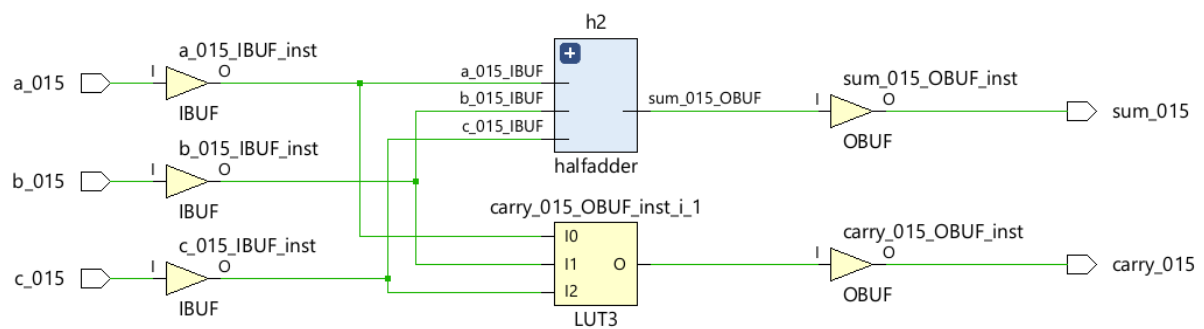Function Verification:**Post synthesis schematic:**

Post power report:

Summary

Power estimation from Synthesized netlist. Activity derived from constraints files, simulation files or vectorless analysis. Note: these early estimates can change after implementation.

Total On-Chip Power: 1.01 W

Design Power Budget: Not

Process: typical

Power Budget Margin: N/A

Junction Temperature: 26.9°C

Thermal Margin: 58.1°C (30.7 W)


Ambient Temperature: 25.0 °C

Effective θ_{JA} : 1.9°C/W

Power supplied to off-chip devices: 0 W

Confidence level: Low

On-Chip Power

 


Post synthesis timing summary:

Name	Slack	Levels	Routes	High Fanout	From	To	Total Delay	Logic Delay	Net Delay	Requirement	Source Clock
Path 1	∞	3	4	2	c_015	carry_015	4.512	3.345	1.167	∞	input port clock
Path 2	∞	3	4	2	c_015	sum_015	4.512	3.345	1.167	∞	input port clock

Post utilization/ area summary:

Reports	Design Runs	Timing	Power	Utilization
Q	≡	≡	%	Hierarchy
Name	^1	Slice LUTs (41000)	Bonded IOB (300)	
full_half	2	5		
h2 (halfadder)	1	0		

Post implementation schematic:

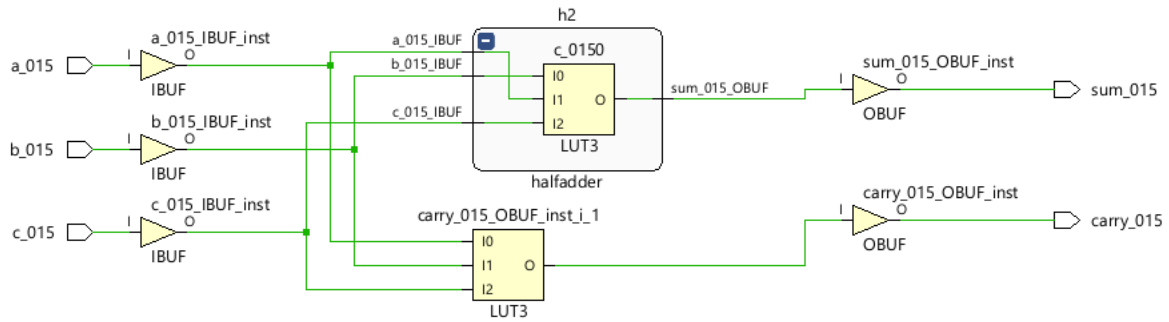


Post implementation power report:

Summary

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power:	0.986 W
Design Power Budget:	Not Specified
Process:	typical
Power Budget Margin:	N/A
Junction Temperature:	26.9°C
Thermal Margin:	58.1°C (30.7 W)
Ambient Temperature:	25.0 °C
Effective θ_{JA} :	1.9°C/W
Power supplied to off-chip devices:	0 W
Confidence level:	Low

On-Chip Power

 

Post implementation timing summary:

Name	Slack	Levels	Routes	High Fanout	From	To	Total Delay	Logic Delay	Net Delay	Requirement	Source Clock
Path 1	∞	3	2	2	a_015	sum_015	5.625	3.272	2.353	∞	input port clock
Path 2	∞	3	2	2	a_015	carry_015	5.622	3.274	2.348	∞	input port clock

Post implementation utilization/ area summary:

Reports	Design Runs	DRC	Power	Timing	Utilization
Hierarchy					
Name	Slice LUTs (41000)	Slice (10250)	LUT as Logic (41000)	Bonded IOB (300)	
full_half	2	1	2	5	
h2 (halfadder)	1	1	1	0	