

Experiment 6

Aim: Write Verilog codes to create a Positive edge trigger JK Flip flop and verify it using a testbench.

Theory:

A JK flip-flop is a sequential logic device with two inputs, J (set) and K (reset), and two outputs, Q (output) and Q' (complement of Q). The flip-flop operates on the rising edge of a clock signal (positive-edge or negative-edge triggered). It can be used to store one bit of information. The primary operations of a JK flip-flop are as follows:

When $J = 0$ and $K = 0$, the flip-flop remains in its current state (no change).

When $J = 0$ and $K = 1$, the flip-flop resets (Q becomes 0).

When $J = 1$ and $K = 0$, the flip-flop sets (Q becomes 1).


When $J = 1$ and $K = 1$, the flip-flop toggles its state (Q' becomes the complement of Q).


JK Flip-Flop Truth Table:

Here is the truth table for a positive-edge triggered JK flip-flop:

J	K	CLK	Q(n)	Q(n+1)
0	0	↑	Q(n)	Q(n)
0	1	↑	Q(n)	0
1	0	↑	Q(n)	1
1	1	↑	Q(n)	$\sim Q(n)$

 In this truth table, Q(n) represents the current state of the flip-flop, Q(n+1) represents the next state, and CLK represents the clock signal.



 **Code:****Behavioural**

```

module jk_flip_flop (
    input CLK,    // Clock input
    input J,      // J input
    input K,      // K input
    output Q,     // Q output
    output Q_bar // Q' (Q bar) output
);

    reg Q, Q_bar; // Flip-flop outputs

    always @(posedge CLK) begin
        if (J & ~K)
            Q <= 1'b1;
        else if (~J & K)
            Q <= 1'b0;
        end

    always @(posedge CLK) begin
        if (J & ~K)
            Q_bar <= 1'b0;
        else if (~J & K)
            Q_bar <= 1'b1;
        end

endmodule

```

Testbench:

```
module testbench;

    reg CLK, J, K;
    wire Q, Q_bar;

    // Instantiate the JK flip-flop
    jk_flip_flop jk_ff (
        .CLK(CLK),
        .J(J),
        .K(K),
        .Q(Q),
        .Q_bar(Q_bar)
    );

    // Clock generation
    always begin
        #5 CLK = ~CLK;
    end

    // Stimulus generation
    initial begin
        CLK = 0;
        J = 0;
        K = 0;

        // Test case 1: Set Q
        J = 1;
        K = 0;
        #10;
        J = 0;
        #10;

        // Test case 2: Reset Q
        J = 0;
        K = 1;
        #10;
        K = 0;
        #10;

        // Test case 3: Toggle Q
        J = 1;
        K = 1;
        #10;
        J = 0;
        #10;
```

```

K = 0;
#10;


$finish;
end

// Display results
always @(posedge CLK) begin
    $display("Time=%0t J=%b K=%b Q=%b Q_bar=%b", $time, J, K, Q,
    Q_bar);
end


endmodule

```


RTL Schematic:

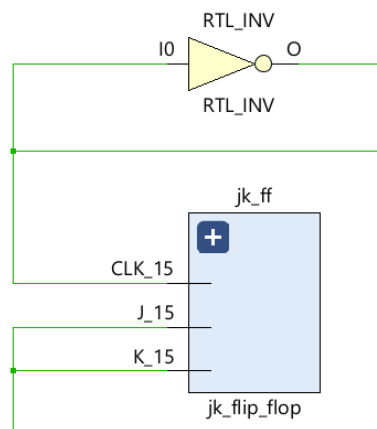


Function Verification:

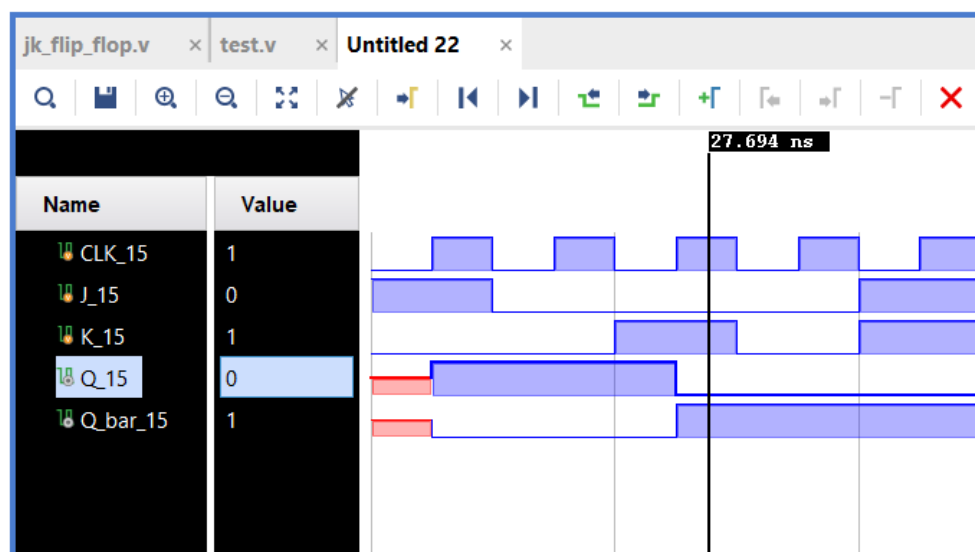

Post synthesis schematic:

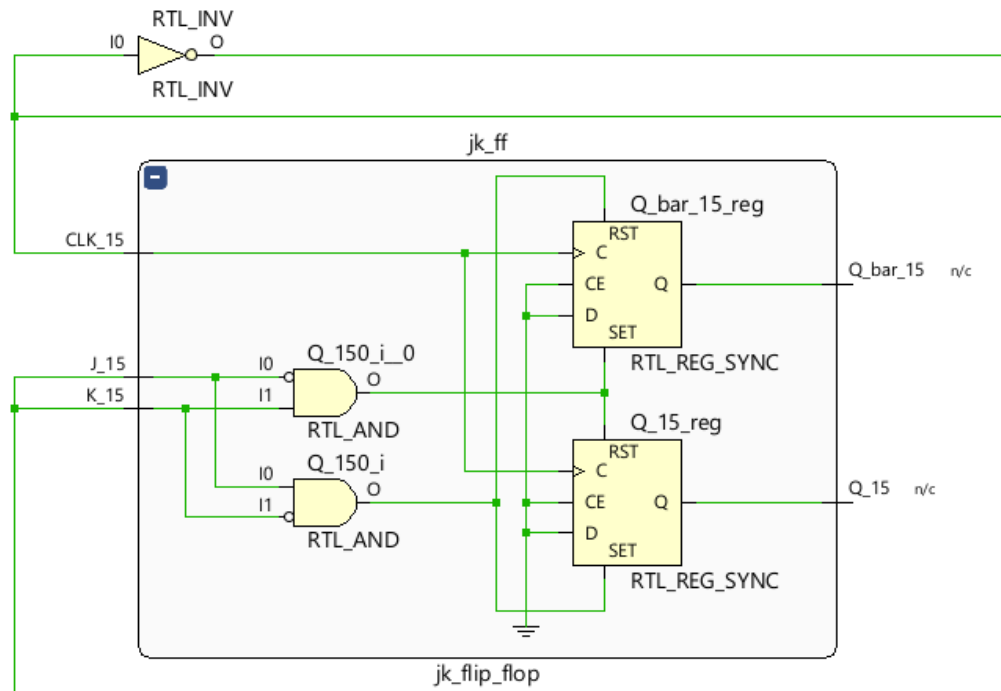

Post power report:

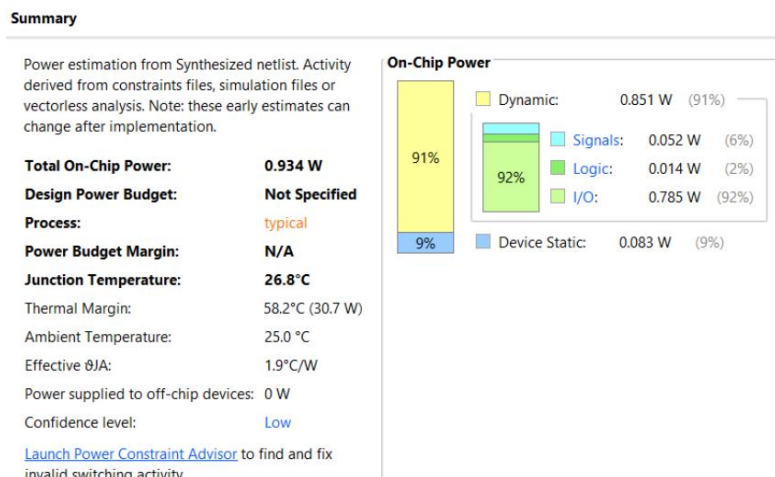

Post synthesis timing summary:

Name	Slack	Levels	Routes	High Fanout	From	To	Total Delay	Logic Delay	Net Delay	Requirement	Source Clock
Path 1	∞	3	2	2	J_15	Q_bar_15	5.836	3.399	2.437	∞	input port clock
Path 2	∞	3	2	2	K_15	Q_15	5.700	3.315	2.384	∞	input port clock

Post utilization/ area summary:

Hierarchy	Name
Summary	testbench
Slice Logic	

Conclusion:

- In this experiment, we written Verilog code for Positive edge trigger JK Flip flop and we have also written code for its testbench and verified its outputs using a testbench.